



UNIT I

Voltage Divider Rule & Current Divider Rule


DC CIRCUITS



Voltage Divider Principle

Voltage divider circuits are used in electronics to supply a *range of voltages needed by a system from a single source.*

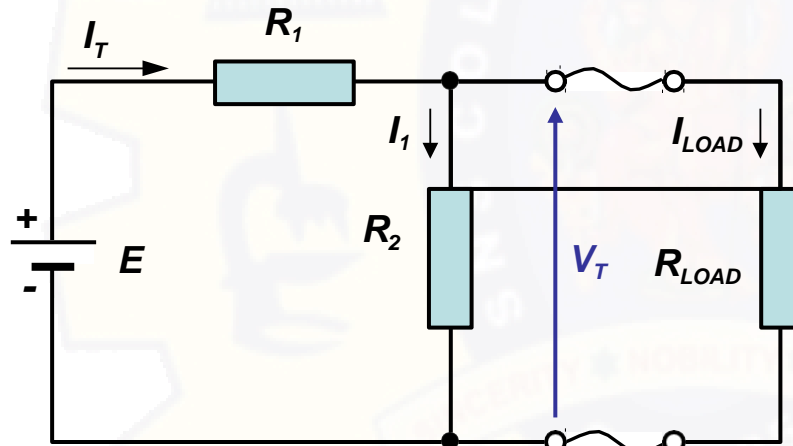The voltage divider uses the principles of Ohm's law to *generate the necessary voltages.*



V_T no load conditions.

$$V_T = E \frac{R_2}{R_1 + R_2}$$

V_T loaded conditions ($I_{LOAD} \ll I_1$)


$$V_T \sim E \frac{R_2}{R_1 + R_2}$$



Voltage Divider Principle

Activity

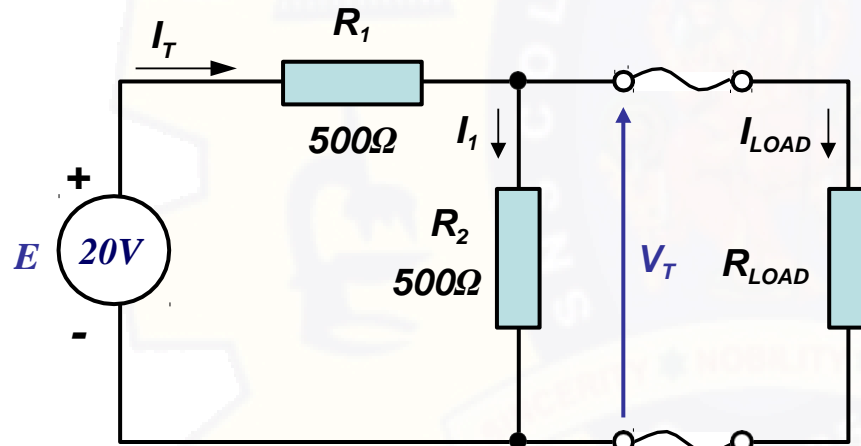Determine the voltage V_T under no load conditions and when a resistance of 2000 ohms is connected.



V_T no load conditions.

$$V_T = E \frac{R_2}{R_1 + R_2}$$

V_T loaded conditions ($I_{LOAD} \ll I_1$)


$$V_T \sim E \frac{R_2}{R_1 + R_2}$$



Divider Networks

Activity

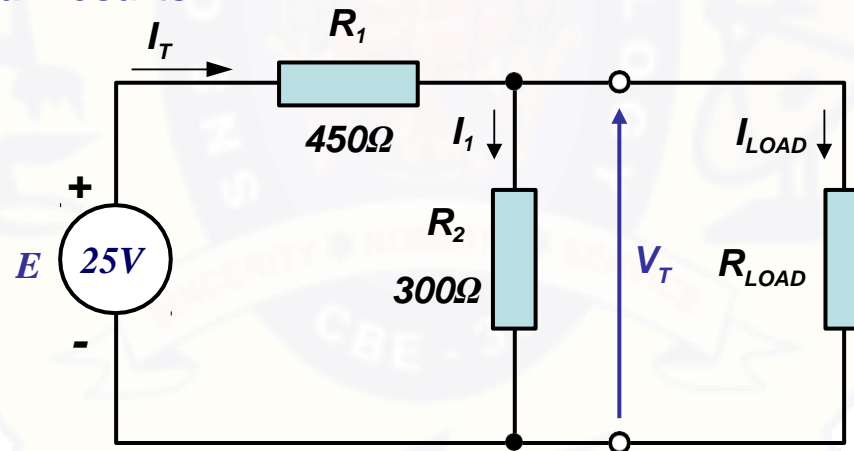1. For the potential divider circuit shown, use the voltage divider principle to evaluate the voltage at V_T a) when open circuit and b) when a load of 1000Ω is connected as shown.
2. If the load resistance (R_{LOAD}) increased to $5k\Omega$ what will be the effect on the voltage V_T .
3. Comment on your results




What is the effect on the voltage (V_T) supplied by the potential divider network as the load (R_{LOAD}) varies.



Current Divider Principle

In parallel circuits the current I_T divides up through the various branch networks, I_1 , I_2 .

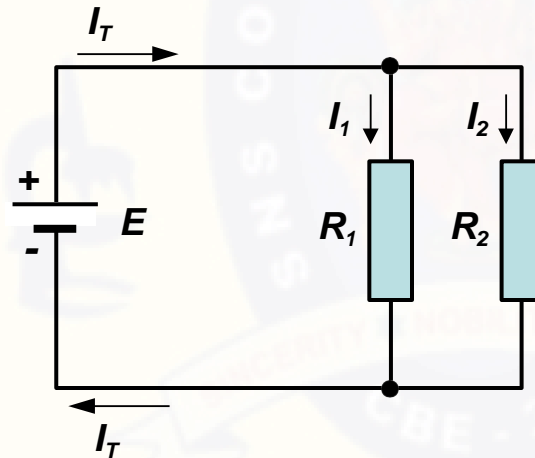The ratio between any two branch currents is the inverse ratio of the branch resistances.



$$I_1 = I_T \frac{R_2}{R_1 + R_2}$$

$$I_2 = I_T \frac{R_1}{R_1 + R_2}$$


This procedure is only suitable where there are two parallel branches.



Current Divider Principle

When there are only two resistances in parallel we can simplify some of the *Ohm's law calculation by use of the current divider principle.*

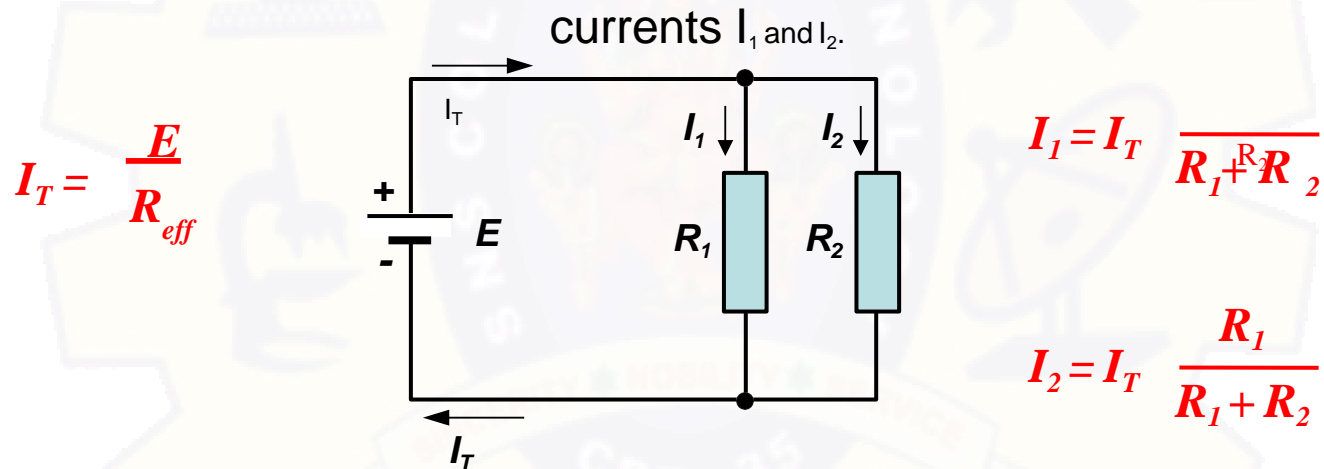The current divider uses the principles of Ohm's law to generate the branch




This procedure is only suitable where there are two parallel branches.



Divider Networks

Activity

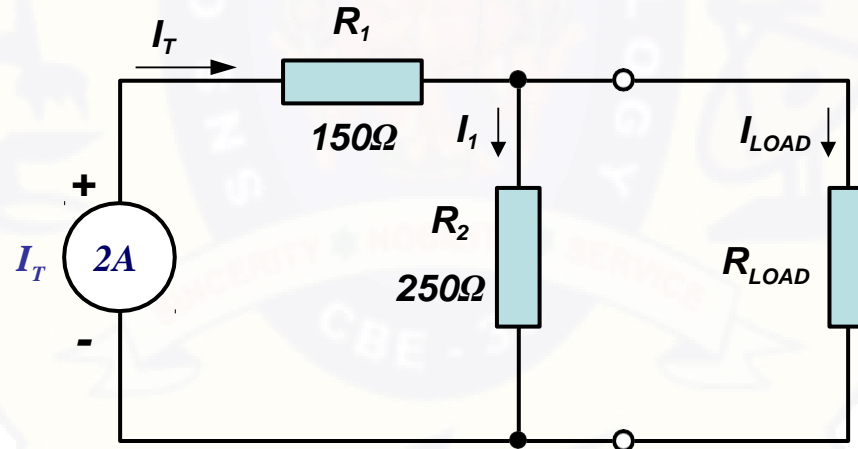1. For the network shown, use the current divider principle to evaluate the branch currents if R_{LOAD} is 1000Ω .
2. If the load resistance (R_{LOAD}) is reduced to 500Ω what current will flow in each branch assuming the source current stays the same at $2A$.
3. Comment on your results.



What is the effect on the branch currents supplied by the 2A current source as the load (R_{LOAD}) varies.