



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade (III Cycle)  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **23ECB202 – LINEAR INTEGRATED CIRCUITS**

II YEAR/ IV SEMESTER  
<sub>1</sub>

#### **UNIT 2 – APPLICATIONS OF OPERATIONAL AMPLIFIERS**

**TOPIC – Clipper**



# Clipper



- A **clipper** is an electronic circuit that produces an output by removing a part of the input above or below a reference value.
- That means, the output of a clipper will be same as that of the input for other than the clipped part.
- The peak to peak amplitude of the output of a clipper will be always less than that of the input.
- The main advantage of clippers is that they eliminate the unwanted noise present in the amplitude of an ac signal.



# TYPES




Clippers can be classified into the following two types based on the clipping portion of the input.

- Positive Clipper
- Negative Clipper


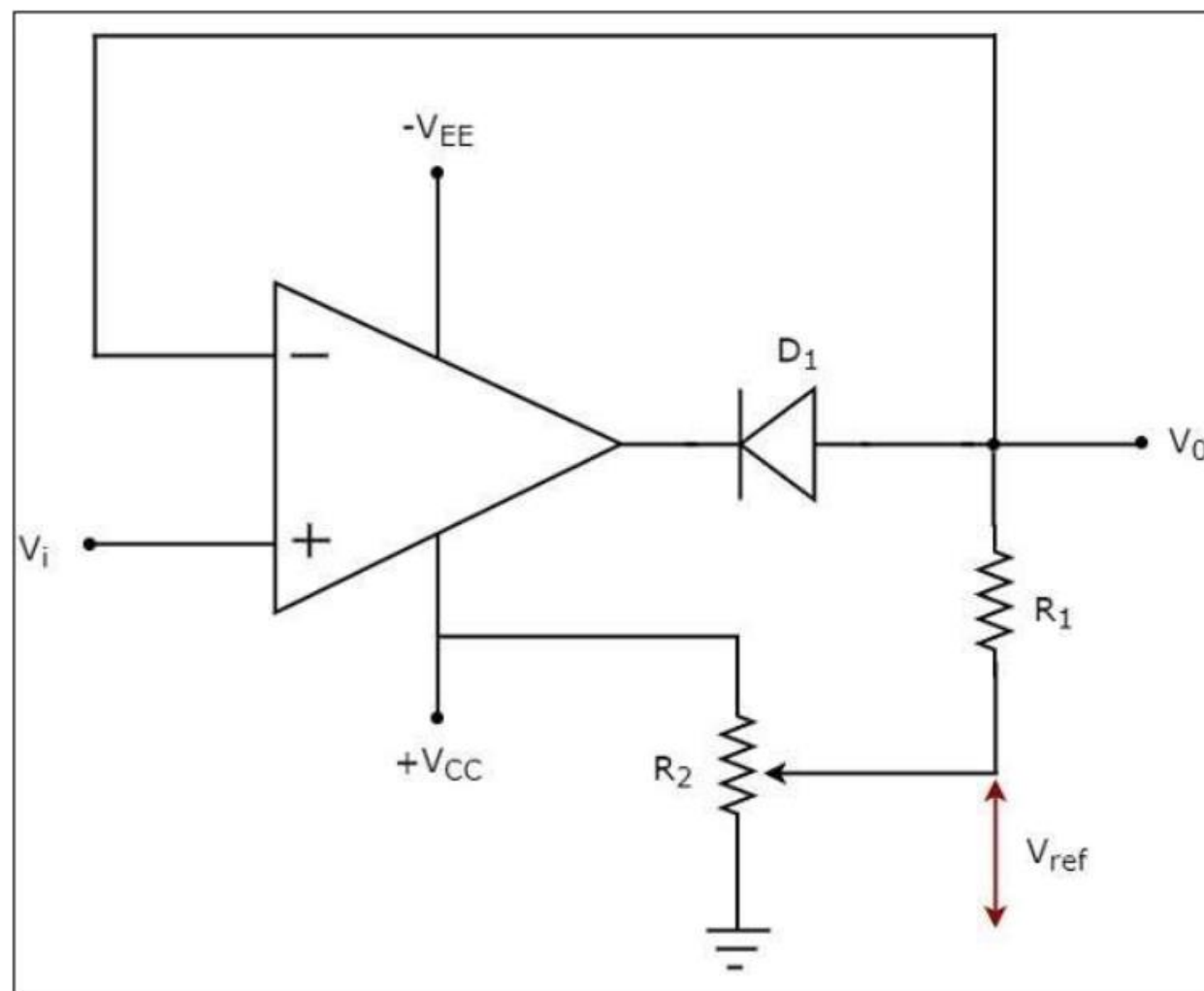
# Positive Clipper

A **positive clipper** is a clipper that clips only the positive portion(s) of the input signal.



- The value of the reference voltage  $V_{ref}$  can be chosen by varying the resistor  $R_2$ .





# Working



- $V_i < V_{ref}$  - diode  $D_1$  conducts - the circuit given above behaves as a **voltage follower**
- Therefore, the output voltage  $V_0$  of the above circuit will be same as that of the input voltage
- $V_i > V_{ref}$  - diode  $D_1$  will be off - op-amp operates in an open loop since the feedback path was open.
- The output voltage will be equal to the reference voltage.




# Waveforms

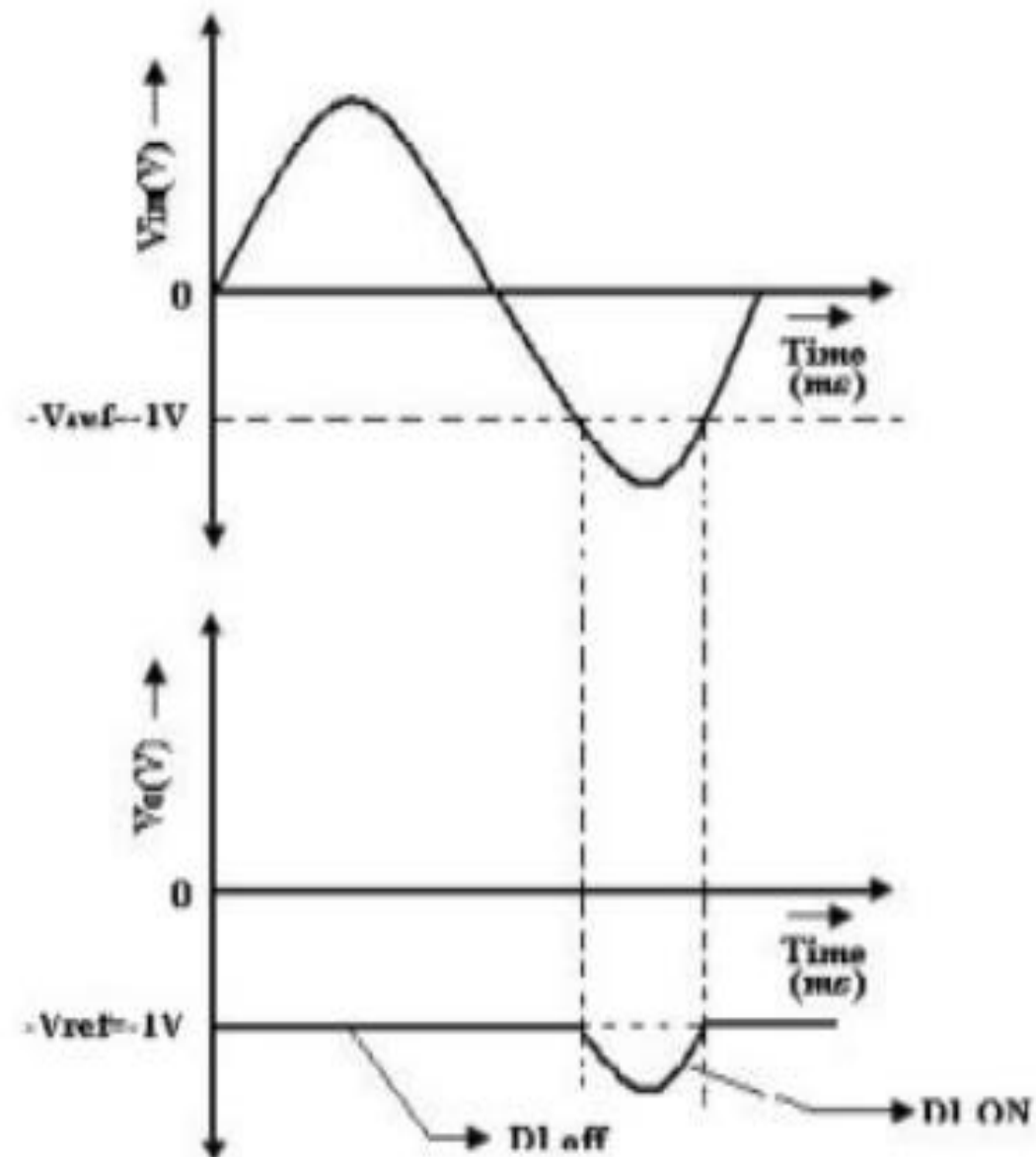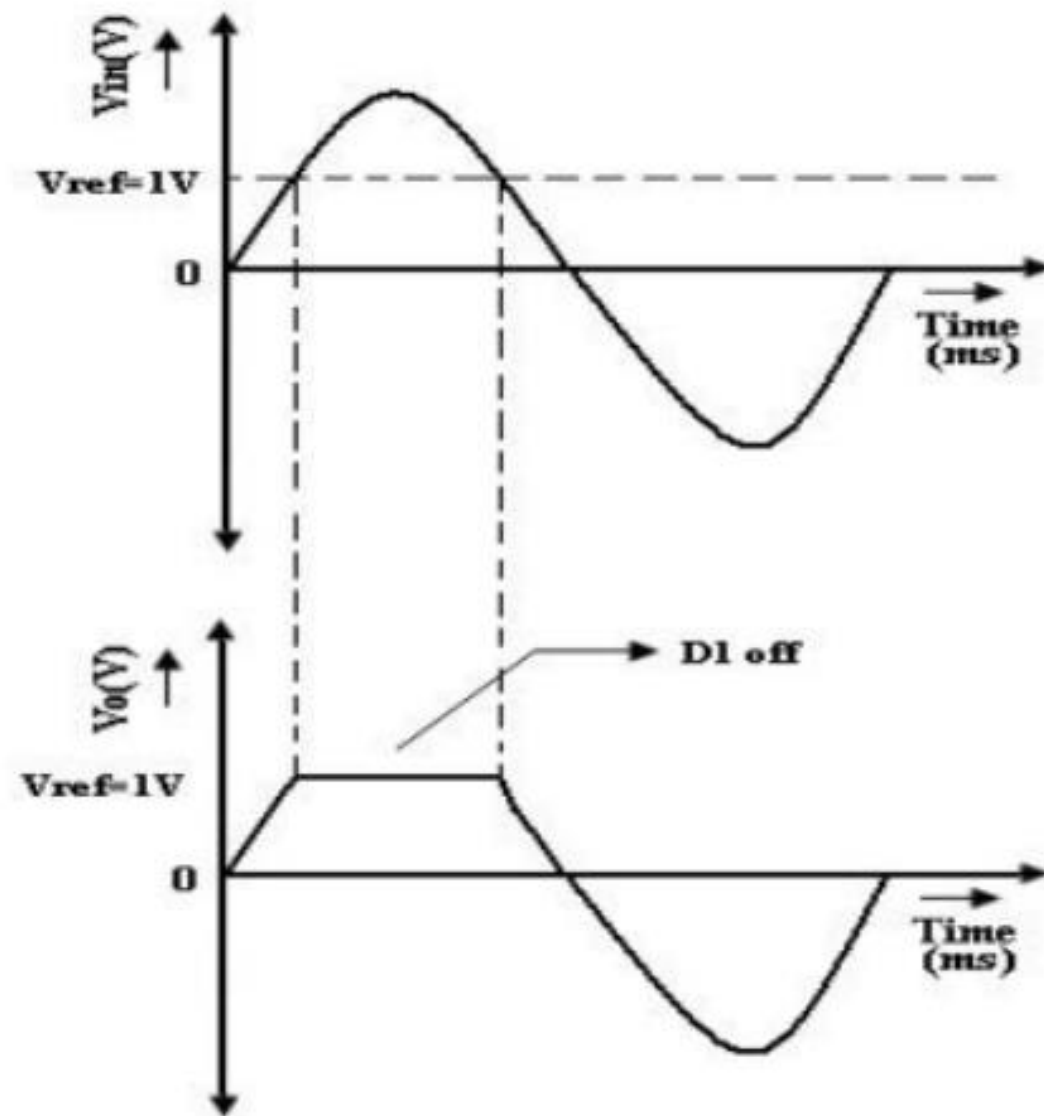


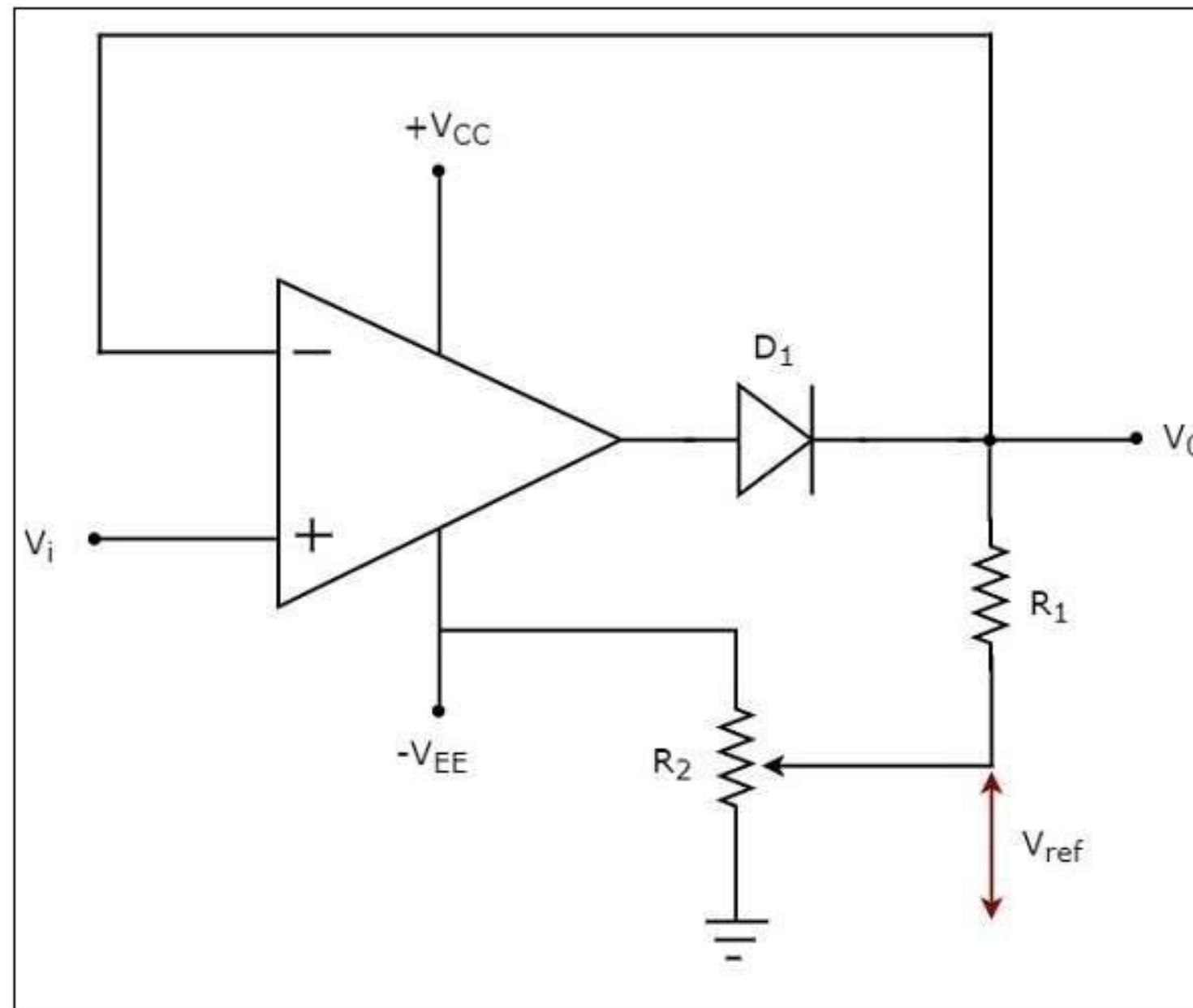
# Negative Clipper

- A **negative clipper** is a clipper that clips only the negative portion(s) of the input signal.







# Working





- $V_i > V_{ref}$  - diode  $D_1$  conducts - the circuit given above behaves as a **voltage follower**
- Therefore, the output voltage  $V_0$  of the above circuit will be same as that of the input voltage
- $V_i < V_{ref}$  - diode  $D_1$  will be off - op-amp operates in an open loop since the feedback path was open.
- The output voltage will be equal to the reference voltage.






# Waveforms

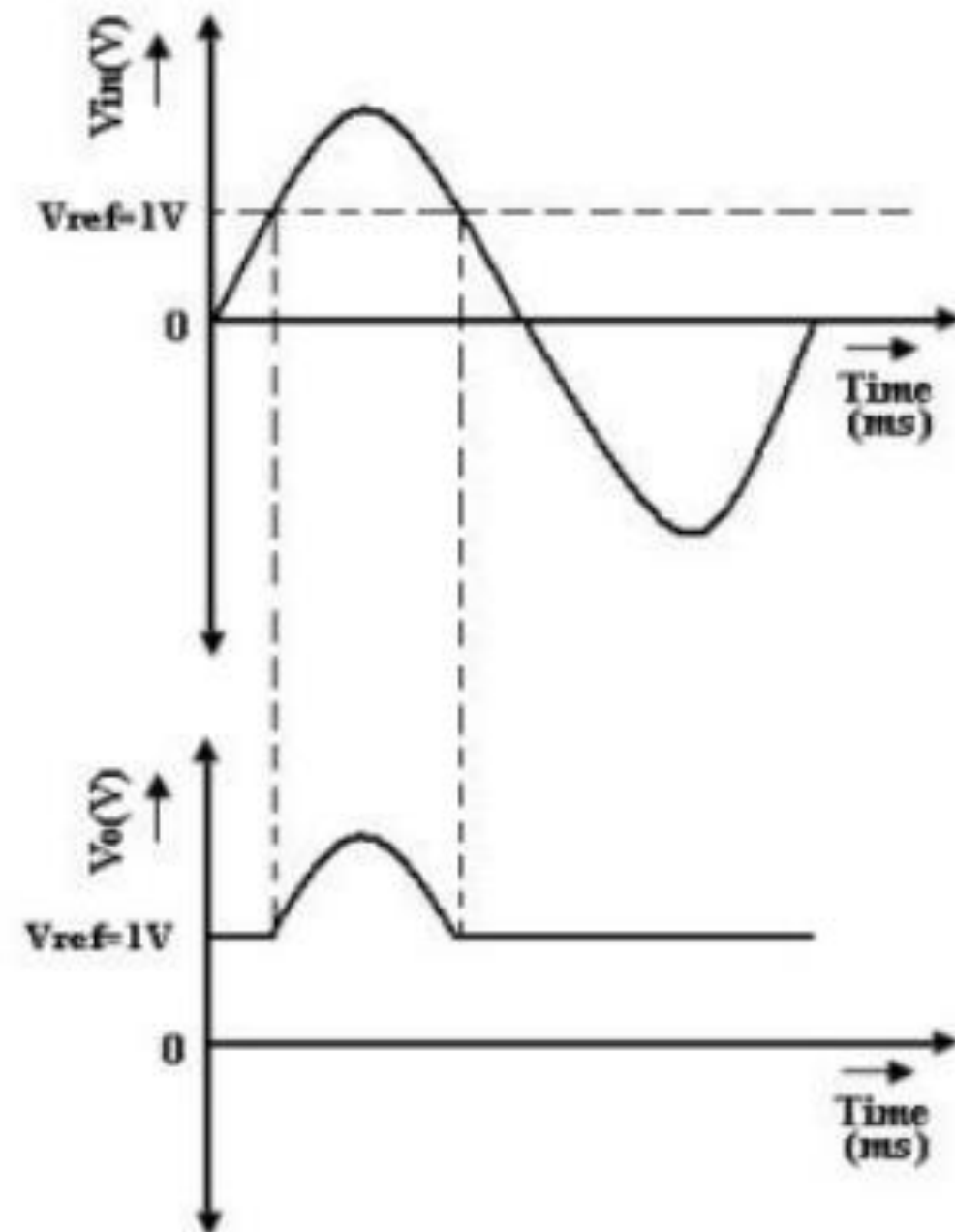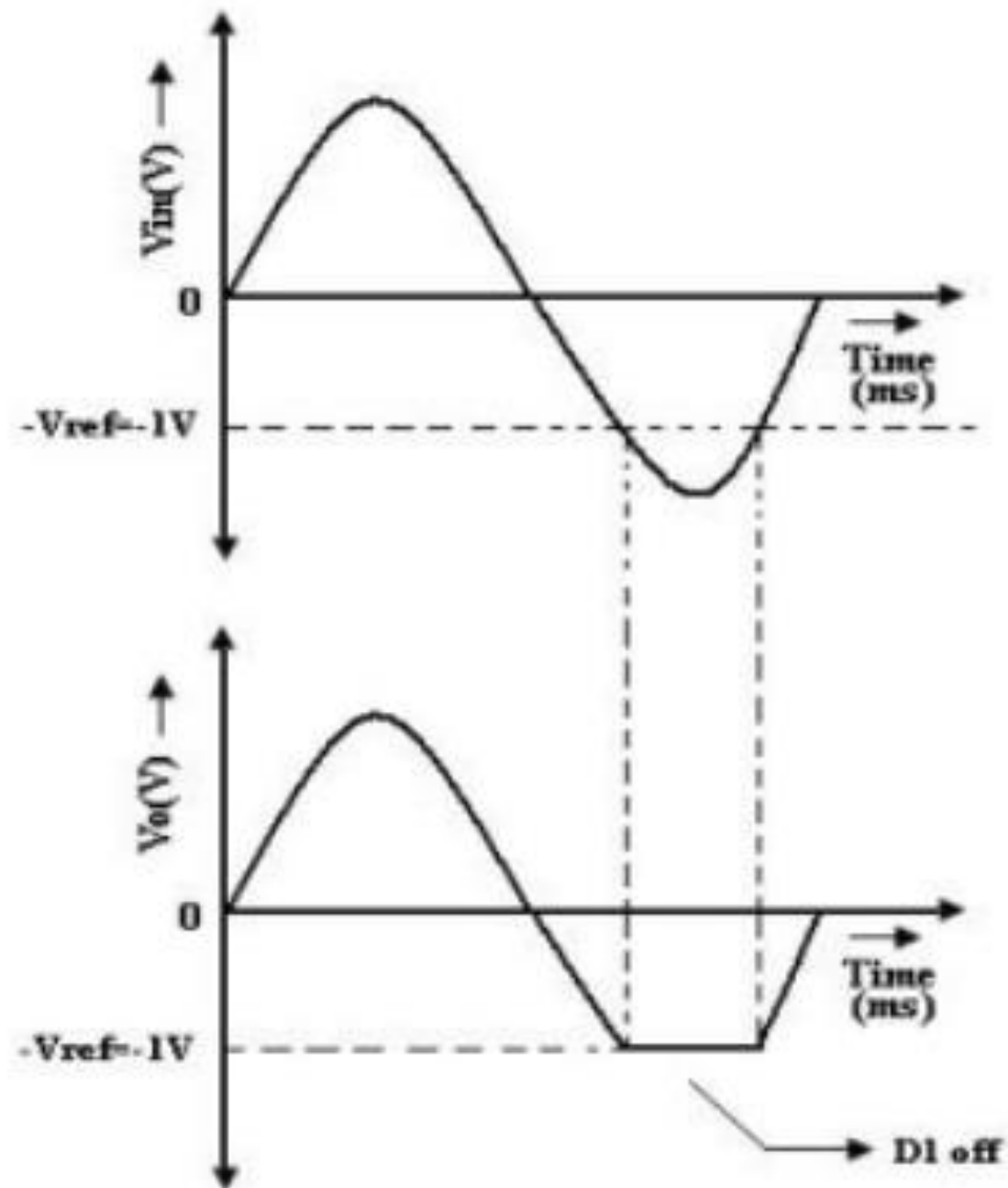



1. The clipping level in op-amp is determined by
    - a) AC supply voltage
    - b) Control voltage
    - c) Reference voltage**
    - d) Input voltage
  2. In a positive clipper, the diode conducts when
    - a)  $V_{in} < V_{ref}$
    - b)  $V_{in} = V_{ref}$**
    - c)  $V_{in} > V_{ref}$
    - d) None of the mentioned
  3. What happens if the input voltage is higher than reference voltage in a positive clipper?
    - a) Output voltage = Reference voltage**
    - b) Output voltage = DC Positive voltage
    - c) Output voltage = Input voltage
    - d) All of the mentioned
- 





**THANK YOU**