



# **SNS COLLEGE OF TECHNOLOGY**

**Coimbatore-35**  
**An Autonomous Institution**



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade (III Cycle)  
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

## **DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING**

### **23ECB202 – LINEAR INTEGRATED CIRCUITS**

II YEAR/ IV SEMESTER  
<sub>1</sub>

#### **UNIT 2 – APPLICATIONS OF OPERATIONAL AMPLIFIERS**

**TOPIC – Precision Rectifier**





# Precision Diode

- The ordinary diodes cannot rectify voltages below the cut-in -voltage of the diode.
- A circuit which can act as an ideal diode or precision signal – processing rectifier circuit for rectifying voltages which are below the level of cut-in voltage of the diode can be designed by placing the diode in the feedback loop of an op-amp.
- Cut-in Voltage is divided by open loop gain of op-amp. So cut-in voltage is virtually eliminated.



# Precision Diode

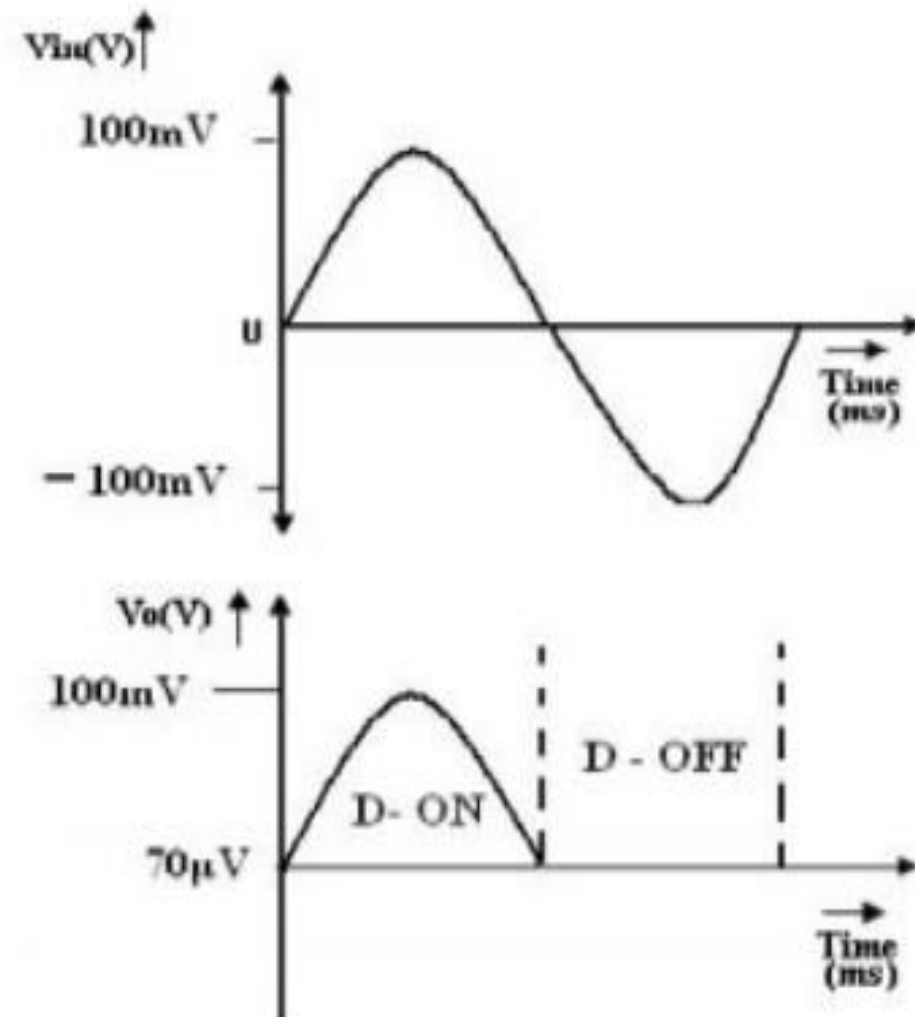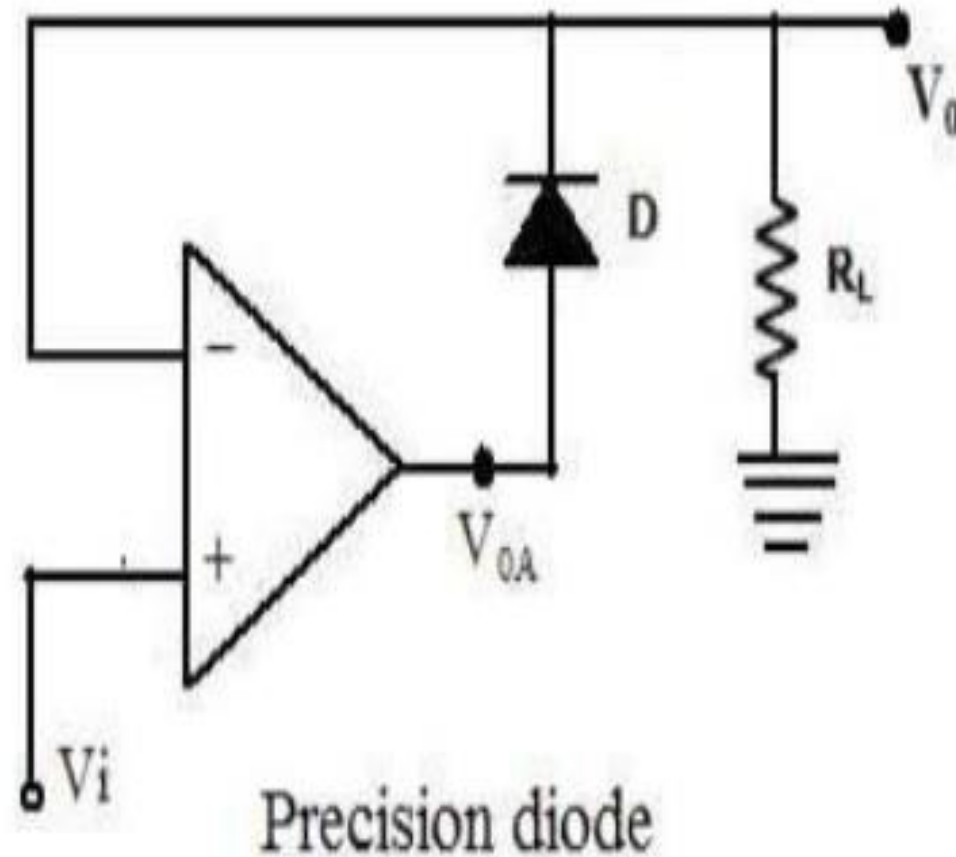

- When  $V_i > V_\gamma / A_{OL}$  Diode conducts – acts as voltage follower.
- When  $V_i < V_\gamma / A_{OL}$  Diode is off – no conduction takes place.



# RECTIFIER



- An electronic circuit, which produces either DC signal or a pulsated DC signal, when an AC signal is applied to it is called as a **rectifier**

## *Types of Rectifiers*

Two types:


**Half wave rectifier**

**Full wave rectifier**


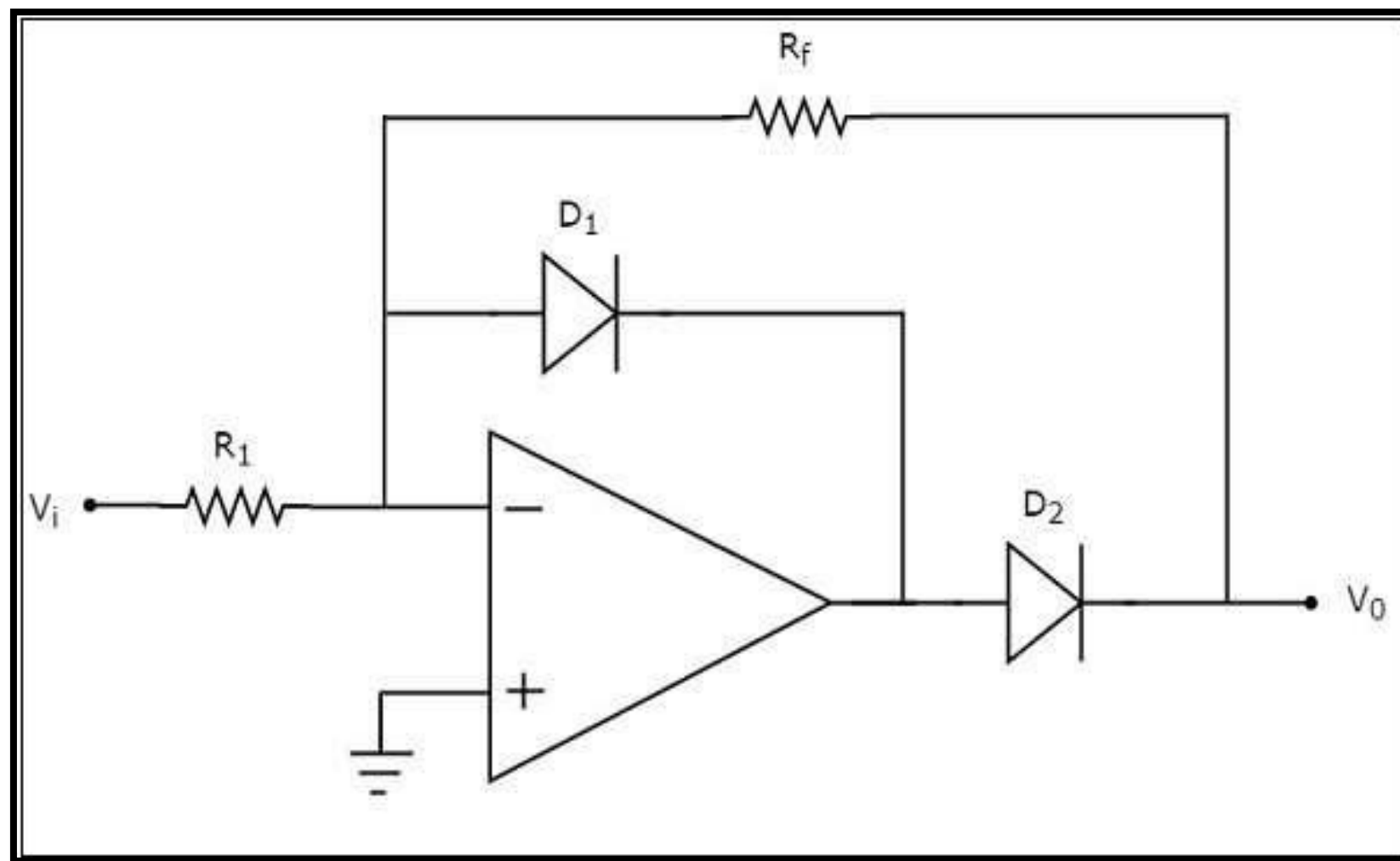
# Half wave Rectifier

- A **half wave rectifier** is a rectifier that produces positive half cycles at the output for one half cycle of the input and zero output for the other half cycle of the input





# Half wave Rectifier

- An inverting amplifier, with two diodes  $D_1$  and  $D_2$
- For the **positive half cycle** of the sinusoidal input, the output of the op-amp will be negative.
- Hence, diode  $D_1$  will be forward biased.
- When diode  $D_1$  is in forward bias, output voltage of the op-amp will be  $-0.7\text{ V}$
- So, diode  $D_2$  will be reverse biased. Hence, the **output voltage** of the above circuit is **zero** volts



# Half wave Rectifier

- There is **no (zero) output** of half wave rectifier for the positive half cycle of a sinusoidal input
- For the **negative half cycle** of sinusoidal input, the output of the op-amp will be positive
- Hence, the diodes  $D_1$  and  $D_2$  will be reverse biased and forward biased respectively
- So, the output voltage of above circuit will be


$$V_0 = -(R_f / R_1) V_1$$

- Therefore, the output of a half wave rectifier will be a **positive half cycle** for a negative half cycle of the sinusoidal input Wave forms


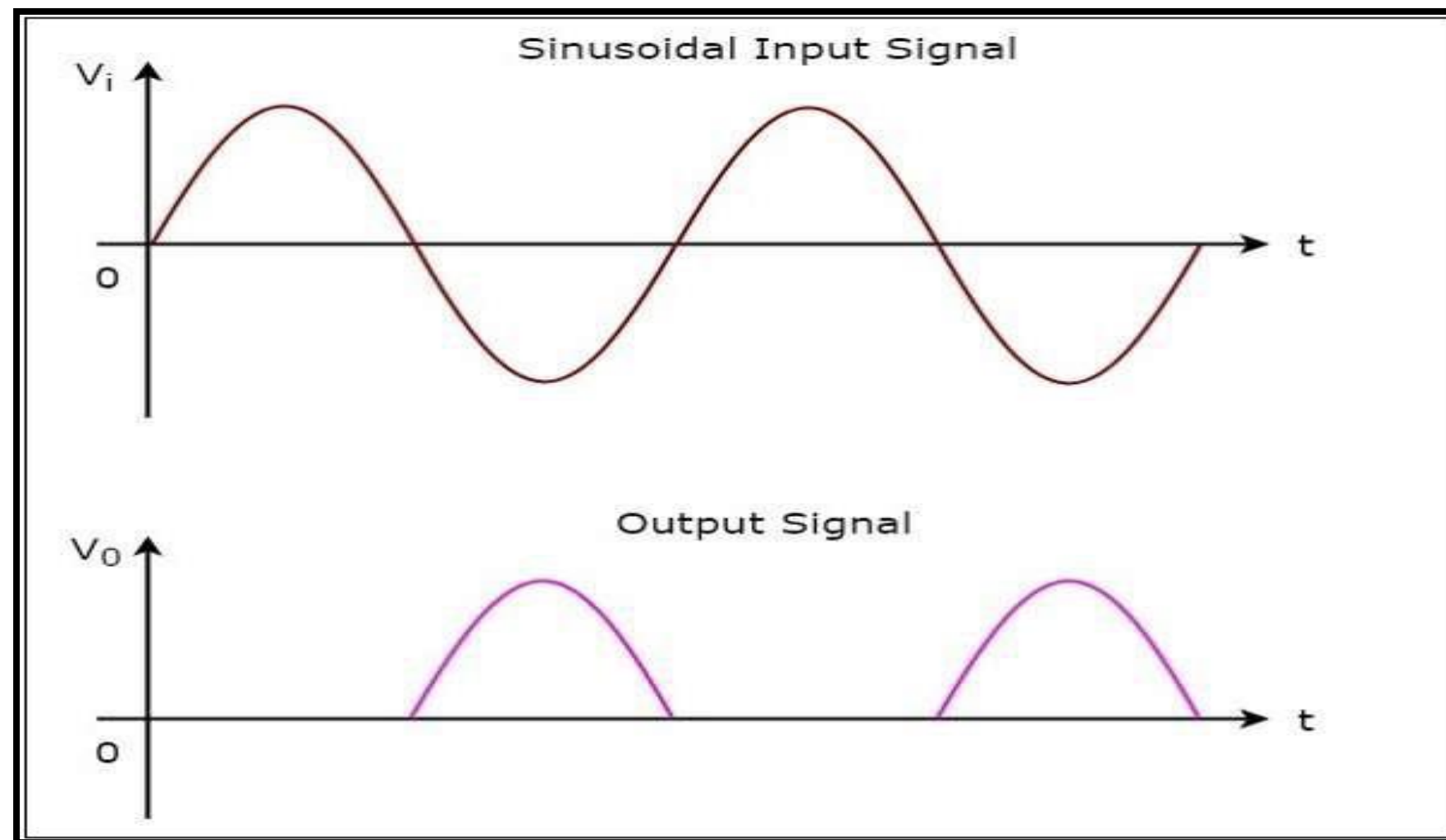
# Half wave Rectifier Waveform


The **input** and **output waveforms** of a half wave rectifier are shown in the following figure




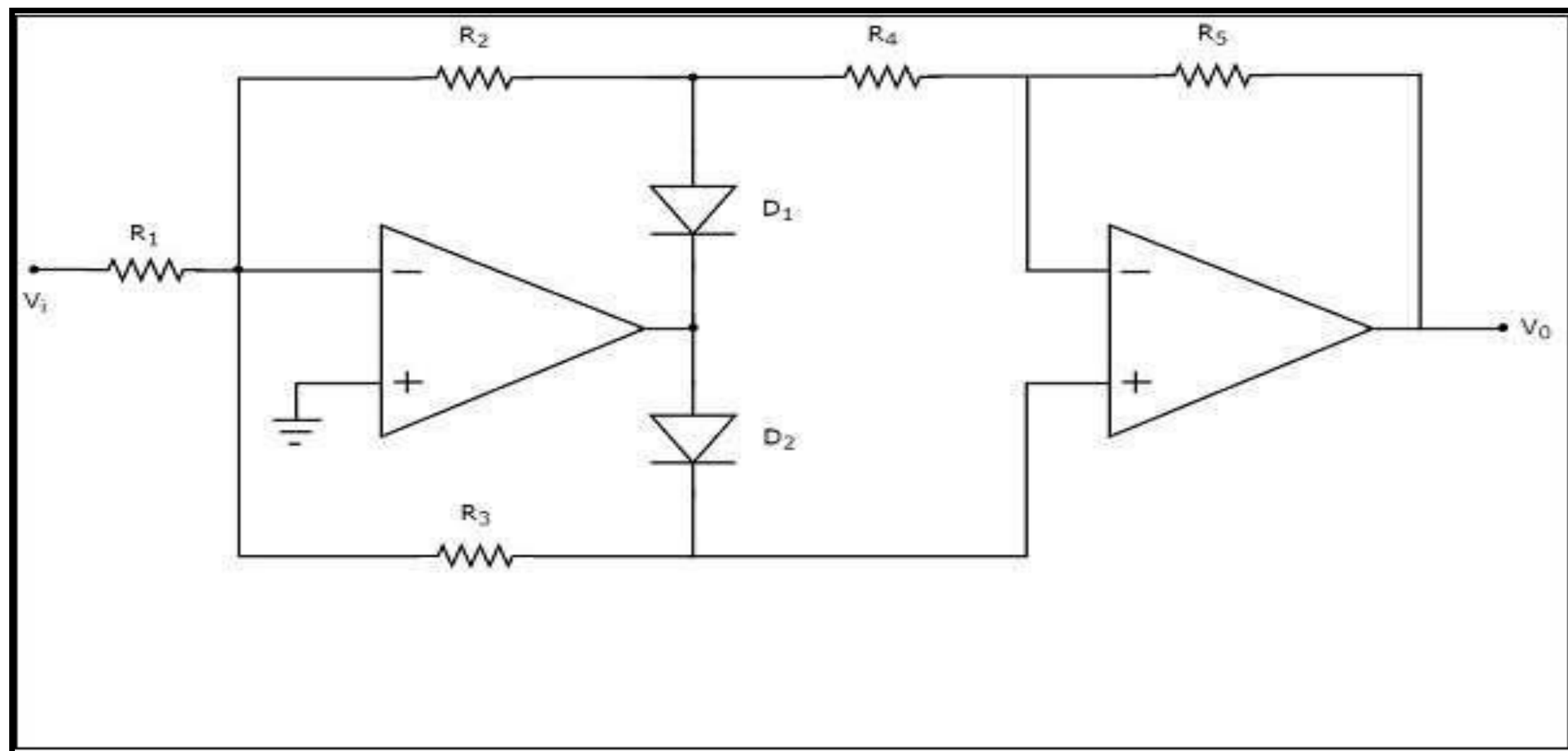
# Full wave Rectifier


- A **full wave rectifier** produces positive half cycles at the output for both positive and negative half cycles of the input.
- The **circuit diagram** of a full wave rectifier is shown below




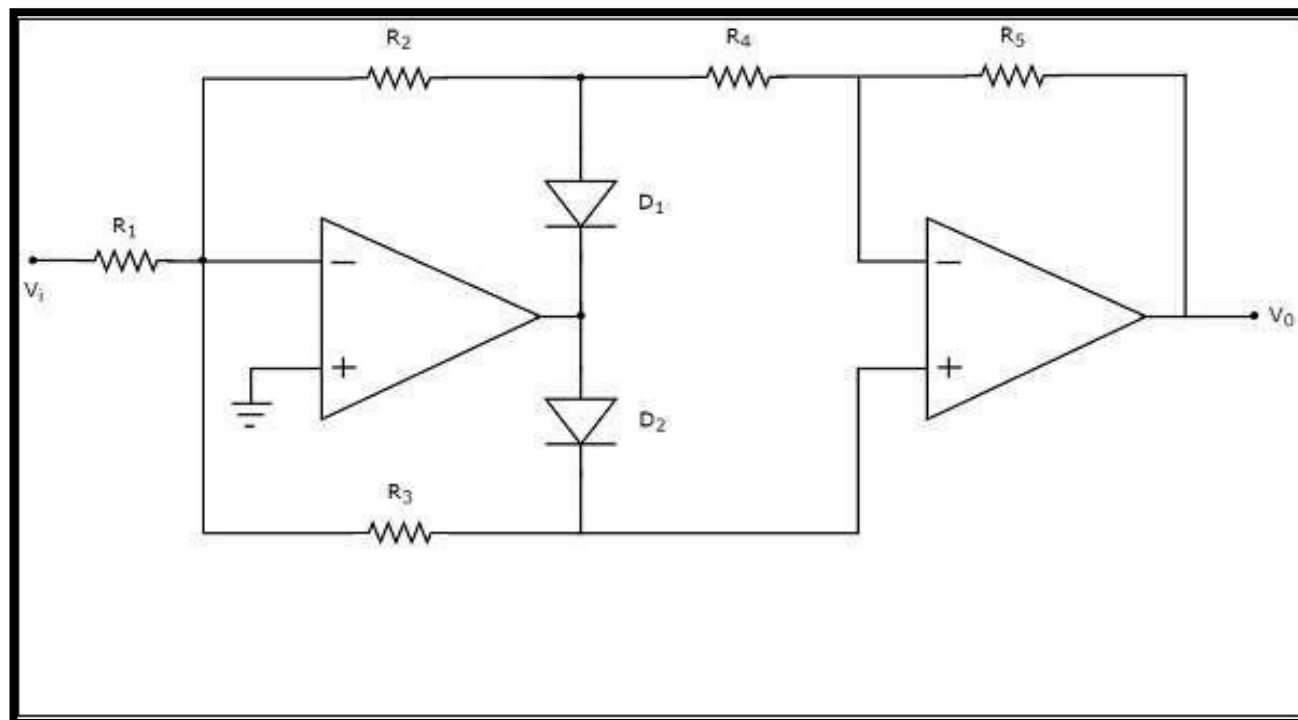
# Full wave Rectifier

- It consists of two op-amps, two diodes,  $D_1$  &  $D_2$  and five resistors,  $R_1$  to  $R_5$
- For the **positive half cycle** of a sinusoidal input, the output of the first op-amp will be negative.
- Hence, diodes  $D_1$  and  $D_2$  will be forward biased and reverse biased respectively
- Then, the output voltage of the first op-amp will be



$$V_{01} = -(R_2/R_1)V_i$$




# Full wave Rectifier

- Observe that the output of the first op-amp is connected to a resistor  $R_4$ , which is connected to the inverting terminal of the second op-amp.
- The voltage present at the non-inverting terminal of second op-amp is 0 V. So, the second op-amp with resistors,  $R_4$  and  $R_5$  acts as an **inverting amplifier**.

$$V_0 = -(R_5/R_4)V_{01}$$

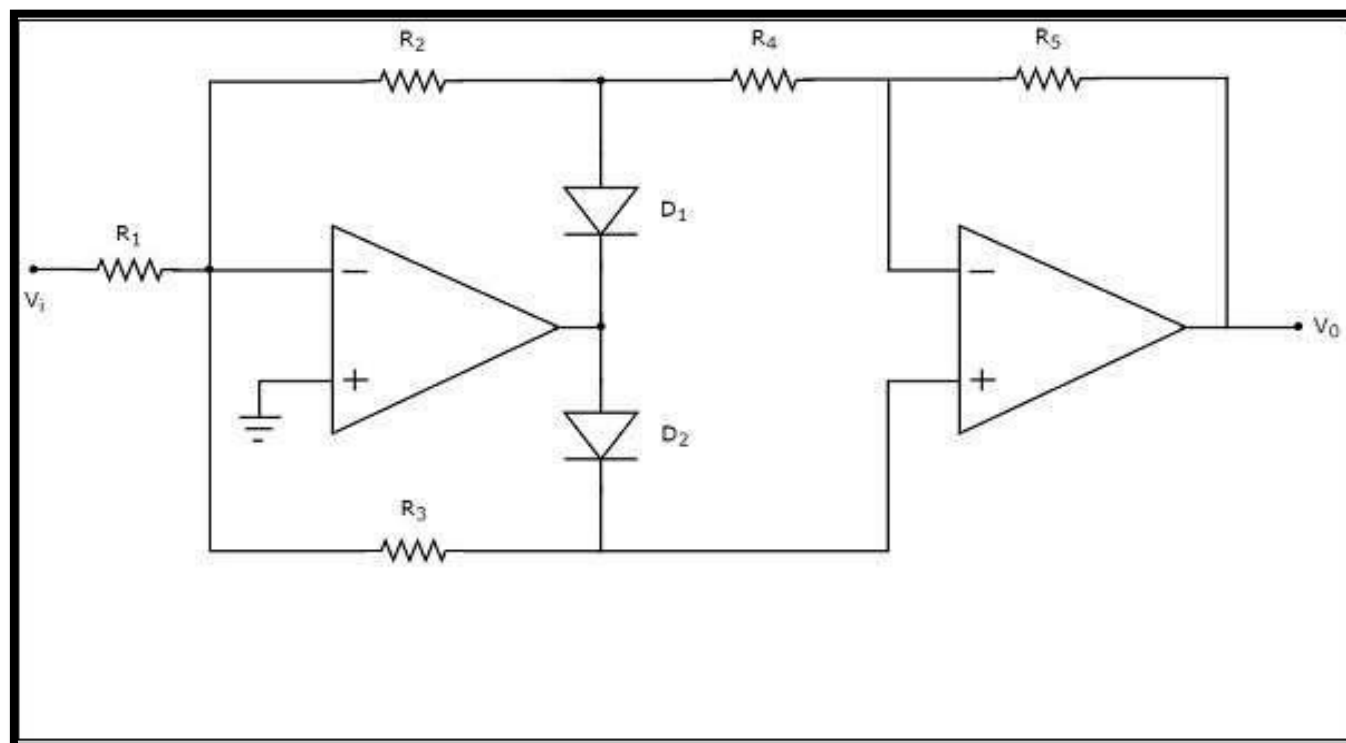**Substituting** the value of  $V_{01}$  in the above equation, we get



$$\begin{aligned} \Rightarrow V_0 &= -(R_5/R_4)\{- (R_2/R_1)V_i\} \\ \Rightarrow V_0 &= (R_2R_5/R_1R_4)V_i \end{aligned}$$



# Full wave Rectifier

- Therefore, the output of a full wave rectifier will be a positive half cycle for the **positive half cycle** of a sinusoidal input.
- In this case, the gain of the output is  $R_2R_5/R_1R_4$
- If we consider  $R_1=R_2=R_4=R_5=R$ , then the gain of the output will be one
- For the **negative half cycle** of a sinusoidal input, the output of the first op-amp will be positive.
- Hence, diodes  $D_1$  and  $D_2$  will be reverse biased and forward biased respectively.




# Full wave Rectifier

- The output voltage of the first op-amp will be

$$V_{01} = -(R_3/R_1)V_i$$

- The output of the first op-amp is directly connected to the non-inverting terminal of the second op-amp
- $R_4$  and  $R_5$  acts as a non-inverting amplifier
- The output voltage of the second op-amp will be  $V_0 = (1 + R_5/R_4)V_{01}$
- Substituting the value of  $V_{01}$  in the above equation,
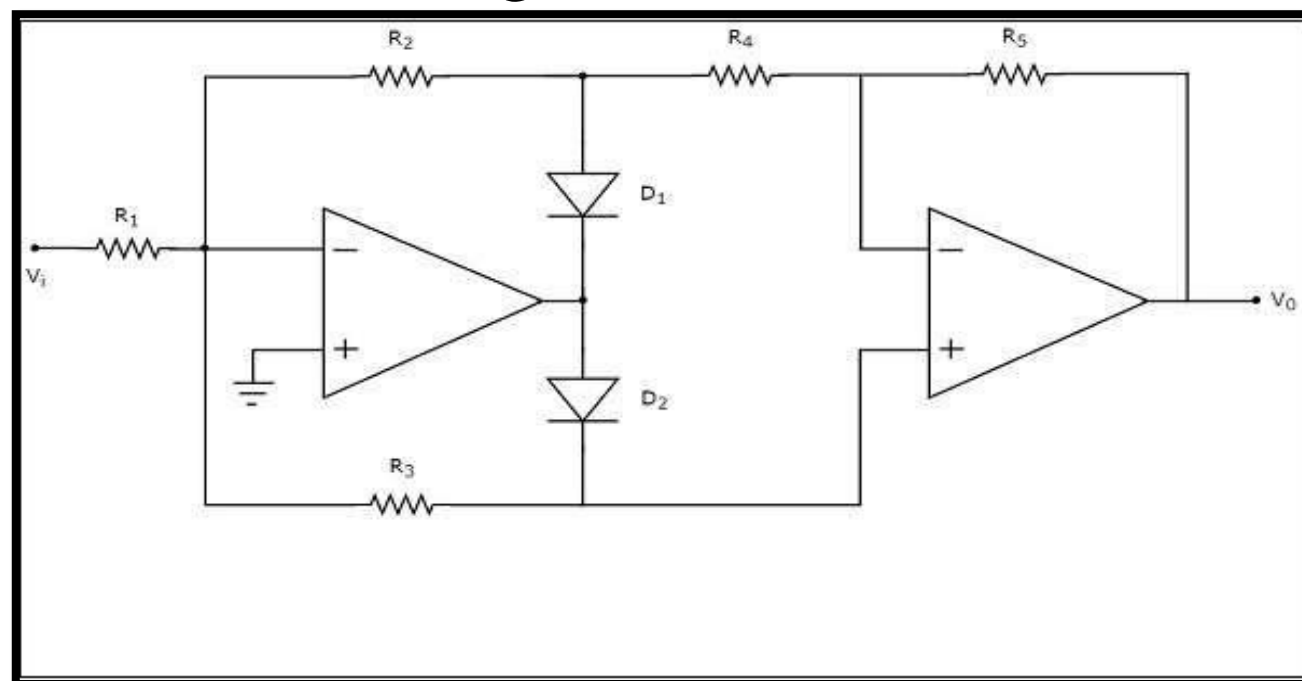
$$\begin{aligned} \Rightarrow V_0 &= (1 + R_5/R_4) \{ -(R_3/R_1)V_i \} \\ \Rightarrow V_0 &= -(R_3/R_1)(1 + R_5/R_4)V_i \end{aligned}$$






# Full wave Rectifier

- The output of a full wave rectifier will be a **positive half cycle** for the negative half cycle of sinusoidal input also
- The magnitude of the gain of the output is  
$$(R3/R1)(1+R5/R4)$$
- If we consider  $R1=2R3=R4=R5=R$  then the gain of the output will be **one**.


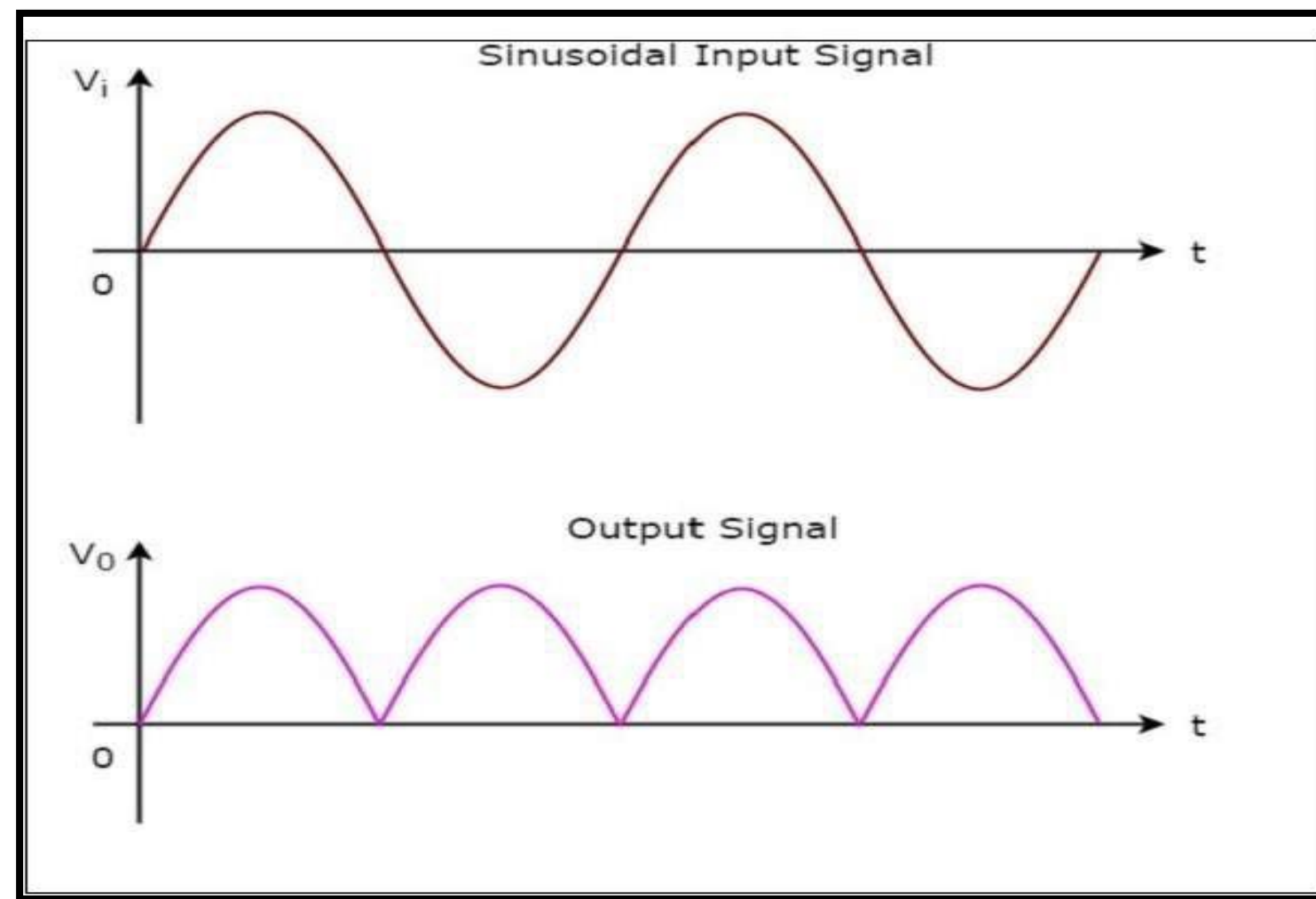
# Full wave Rectifier

The **input** and **output waveforms** of a full wave rectifier





# Assessment

1. In a full wave rectifier, the current in each diode flows for
  - a. whole cycle of the input signal
  - b. half cycle of the input signal**
  - c. more than half cycle of the input signal
  - d. none of these
  
2. In a full wave rectifier, if the input frequency is 50 Hz, then output frequency will be
  - a. 50 Hz
  - b. 75 Hz
  - c. 100 Hz**
  - d. 200 Hz





**THANK YOU**