



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade (III Cycle)
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB202 – LINEAR INTEGRATED CIRCUITS

II YEAR/ IV SEMESTER
1

UNIT 3 – WAVEFORM GENERATORS AND VOLTAGE REGULATORS



TOPIC – Comparator



Comparator



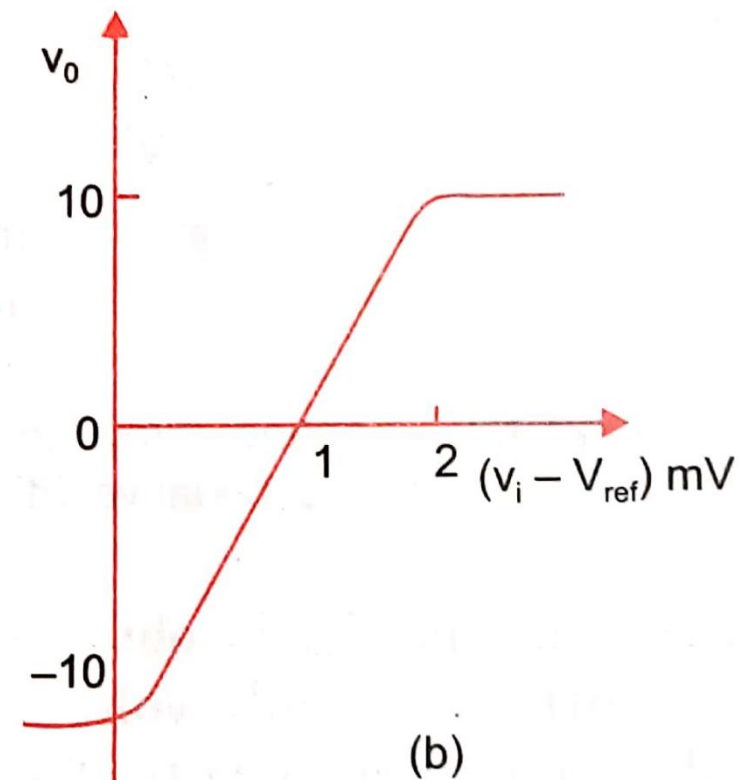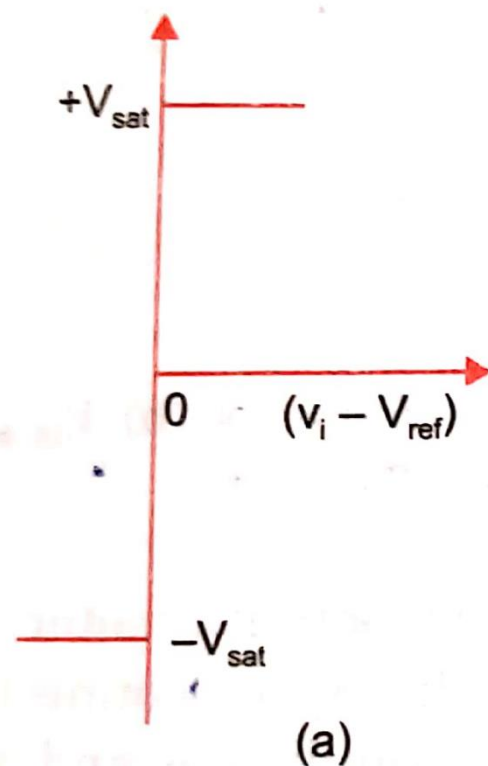- A comparator is a circuit which compares a signal voltage applied at one input of an op-amp with a known reference voltage at the other input.
- It is basically an open loop op amp with output $+V_{sat}$ or $-V_{sat}$ as shown in ideal characteristics.





TYPES




There are basically two types of comparators.

1. Non-inverting comparator
2. Inverting comparator



Non-inverting comparator

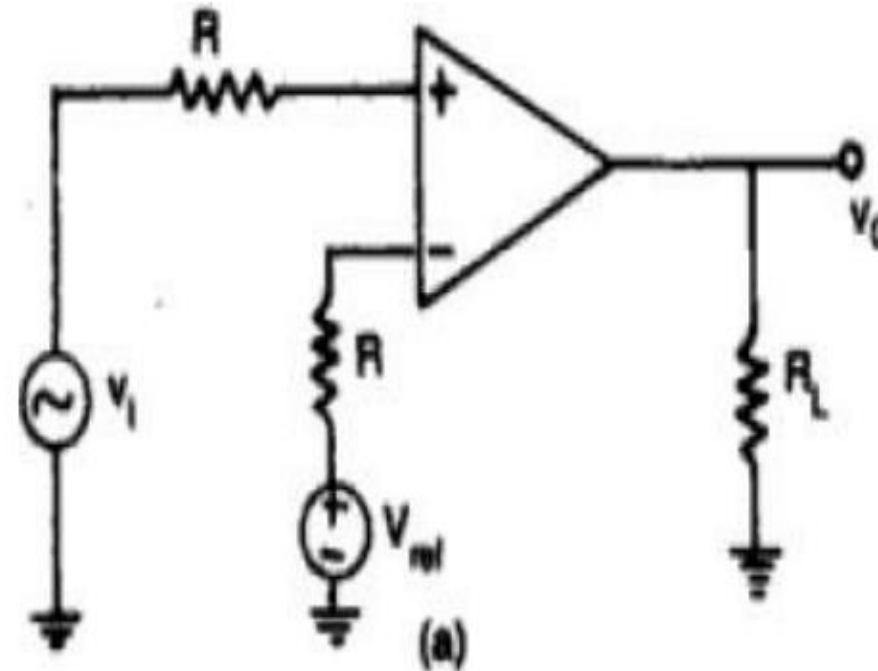


- A fixed reference voltage V_{ref} is applied to $(-)$ input and a time varying signal V_i is applied to $(+)$ input.
- There are 3 conditions for a comparator.
- $V_i < V_{ref}$, $V_o = -V_{sat}$
- $V_i > V_{ref}$, $V_o = +V_{sat}$
- $V_i = V_{ref}$ - changes the state of op-amp



Non-inverting comparator



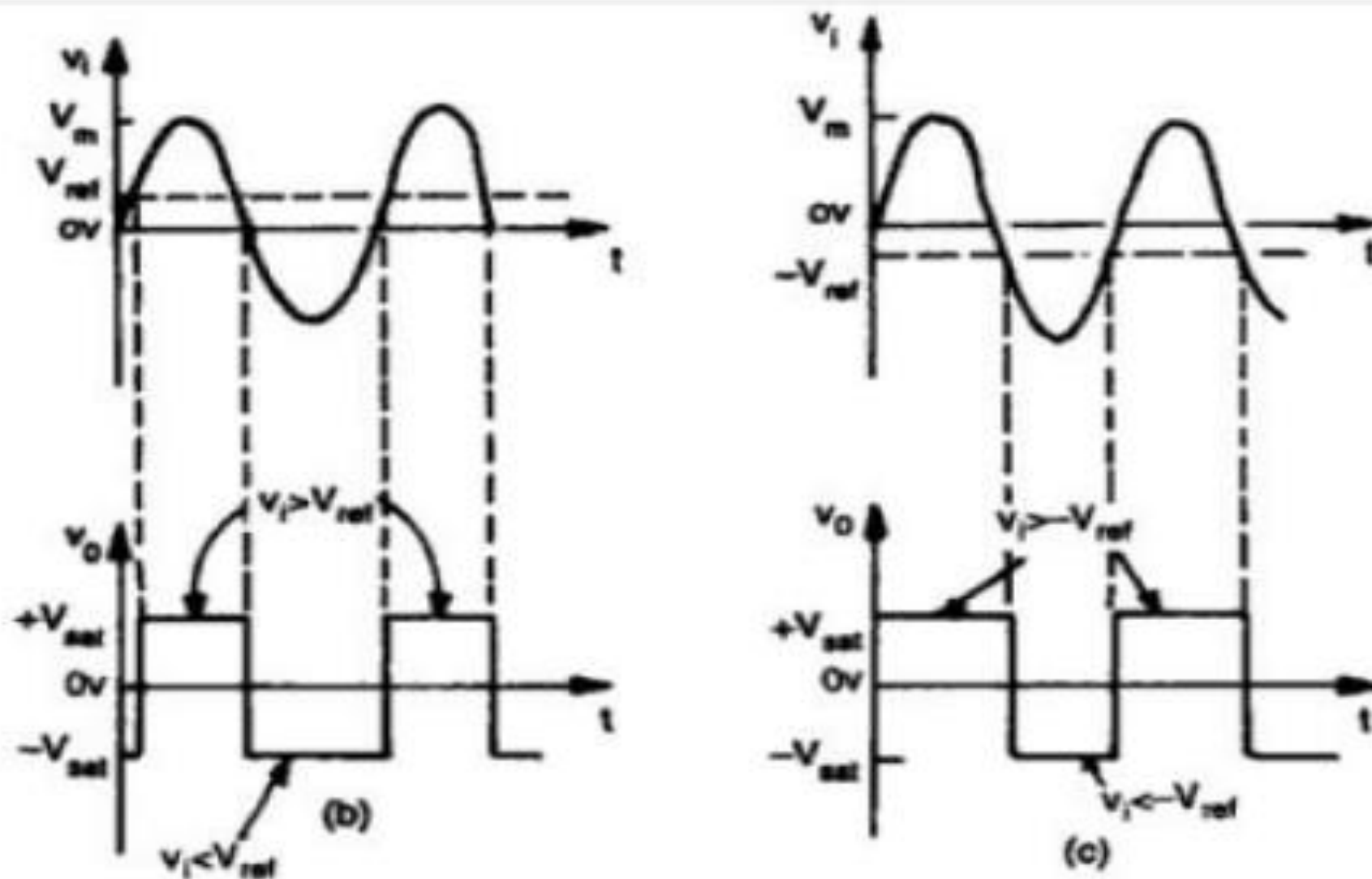The output waveform for a sinusoidal input signal applied to the +ve input is shown in figure for +ve and –ve V_{ref} respectively





Inverting comparator

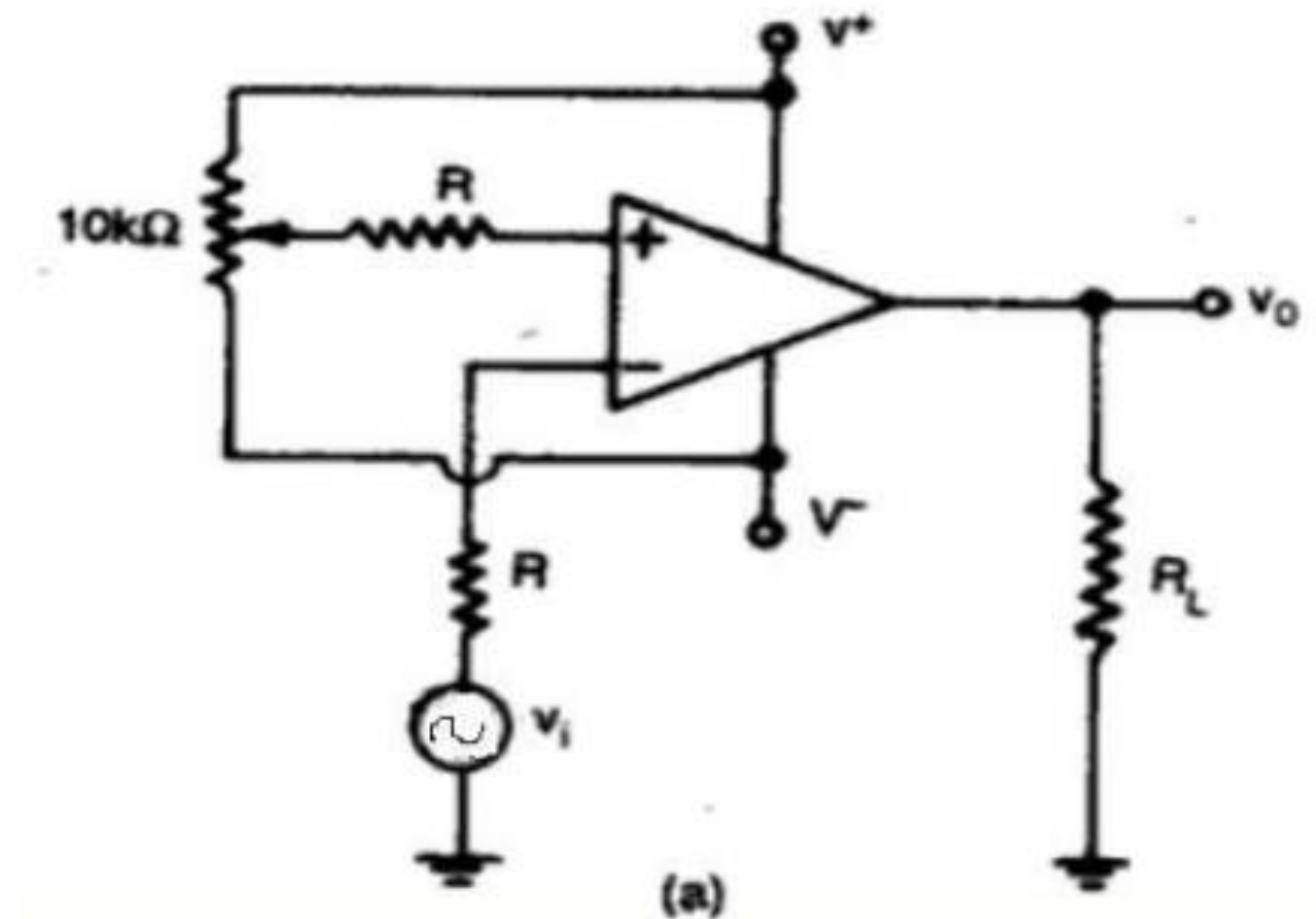


Figure shows a practical inverting comparator in which the reference voltage V_{ref} is applied to the (+) input and V_i is applied to the – ve input.



Inverting comparator

For a sinusoidal input signal, the output waveform is shown in figure for V_{ref} +ve and -ve respectively.

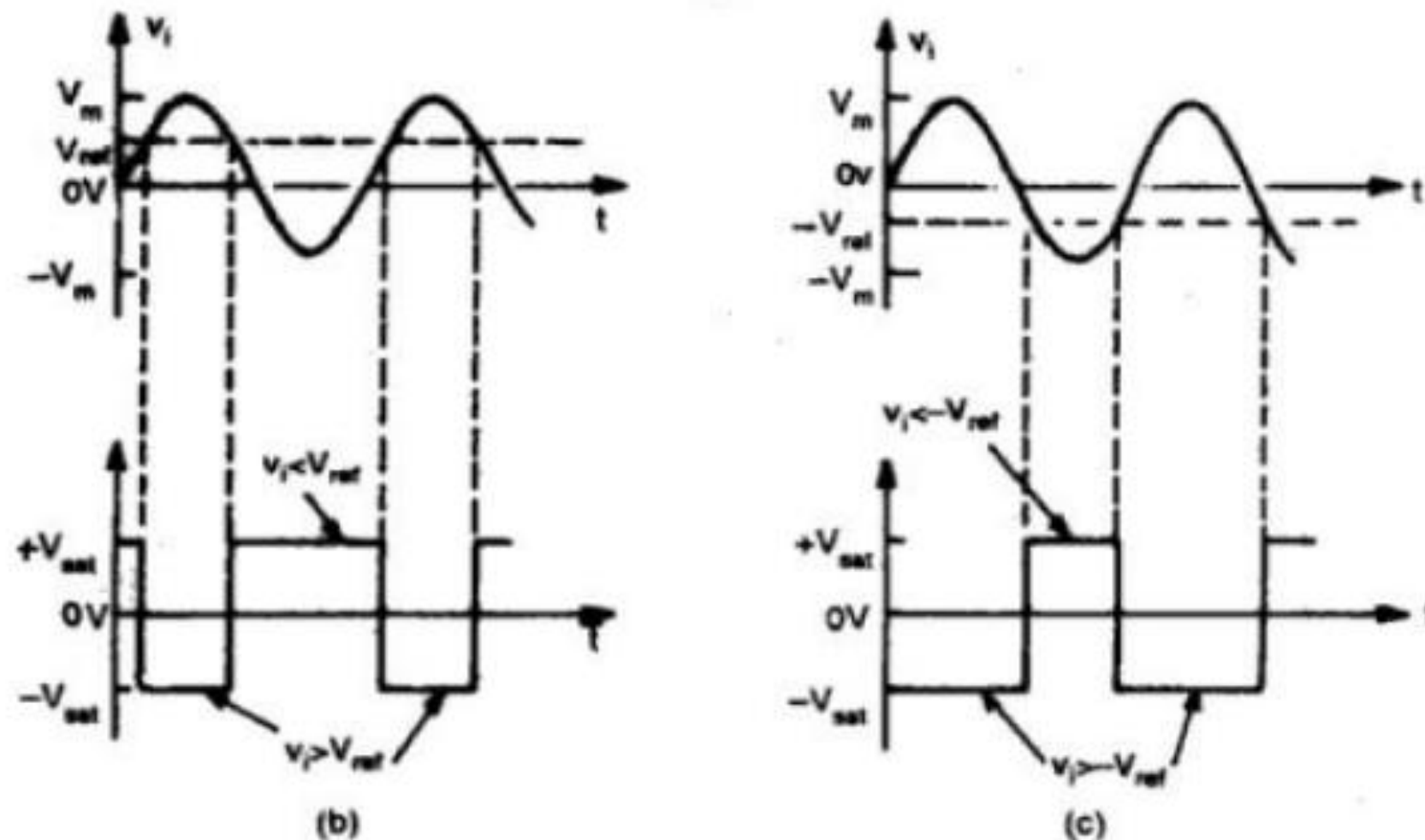


Fig. 5.3 (a) Inverting comparator. Input and output waveforms (b) $V_{ref} > 0$
(c) $V_{ref} < 0$



Applications



Some important applications of comparator are

- Zero crossing detector
- Window detector
- Time marker generator
- Phase meter.



Zero crossing detector

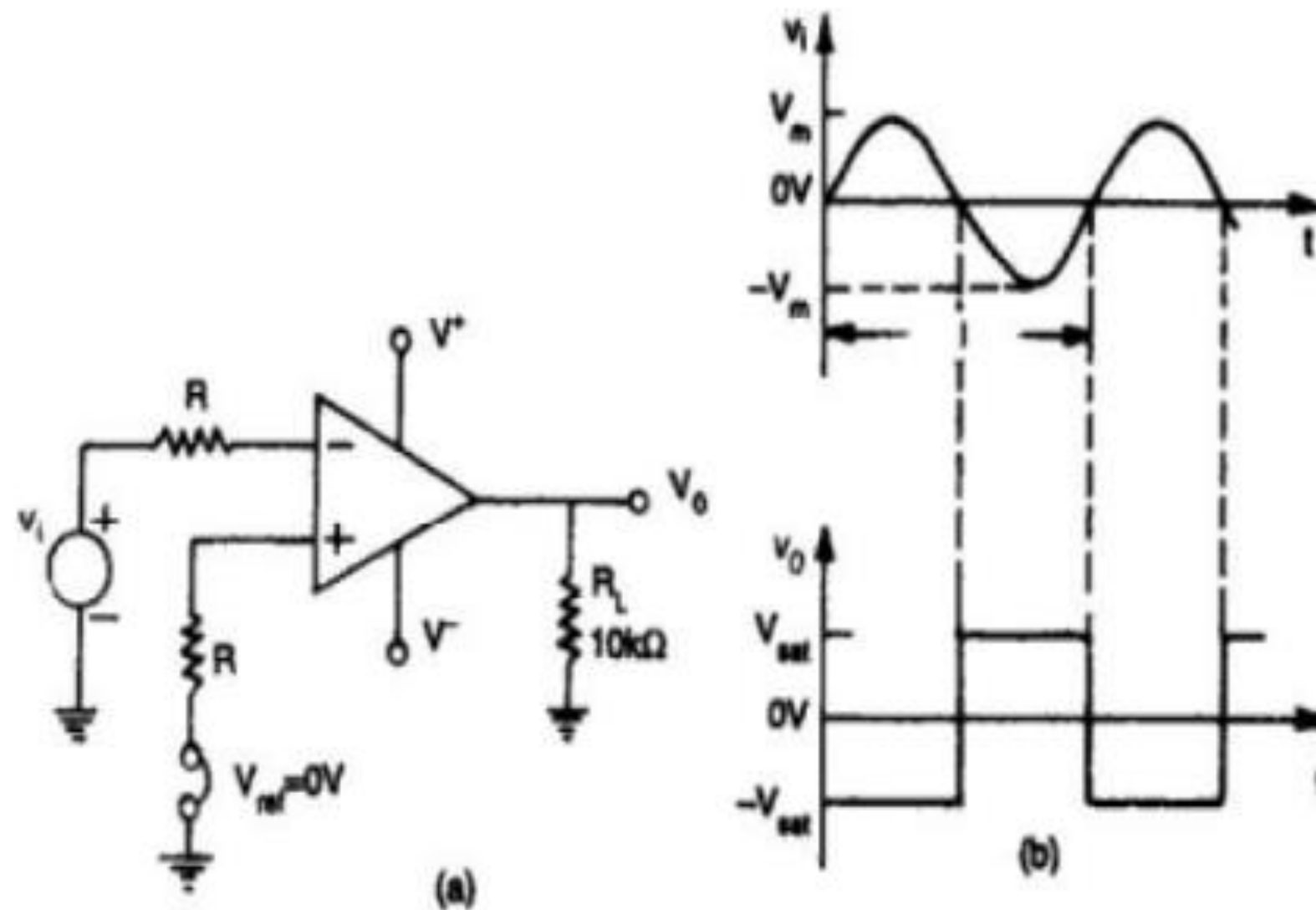


Fig. 5.4 (a) Zero crossing detector (b) Input and output waveforms

The circuit is also called as a sine to square wave generator.



Assessment



1. Depending on the value of input and reference voltage a comparator can be named as

- a) Voltage follower
- b) Digital to analog converter
- c) Schmitt trigger
- d) Voltage level detector**



2. Zero crossing detectors is also called as

- a) Square to sine wave generator
- b) Sine to square wave generator**
- c) Sine to triangular wave generator
- d) All of the mentioned



THANK YOU