



## UNIT I

# Voltage Divider Rule & Current Divider Rule


## DC CIRCUITS


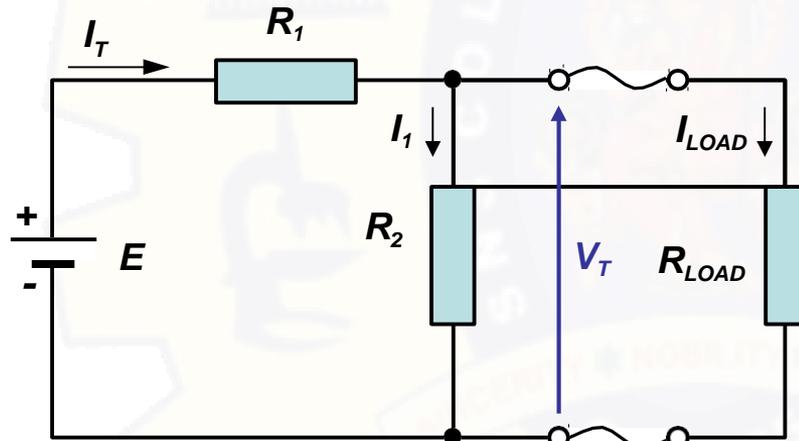
# Voltage Divider Principle

Voltage divider circuits are used in electronics to supply a *range of voltages needed by a system from a single source.*

The voltage divider uses the principles of Ohm's law to *generate the necessary voltages.*



*$V_T$  no load conditions.*

$$V_T = E \frac{R_2}{R_1 + R_2}$$

*$V_T$  loaded conditions ( $I_{LOAD} \ll I_1$ )*

$$V_T \sim E \frac{R_2}{R_1 + R_2}$$


For good stability current  $I_1$  must be at least ten times that flowing in the load.



# Voltage Divider Principle
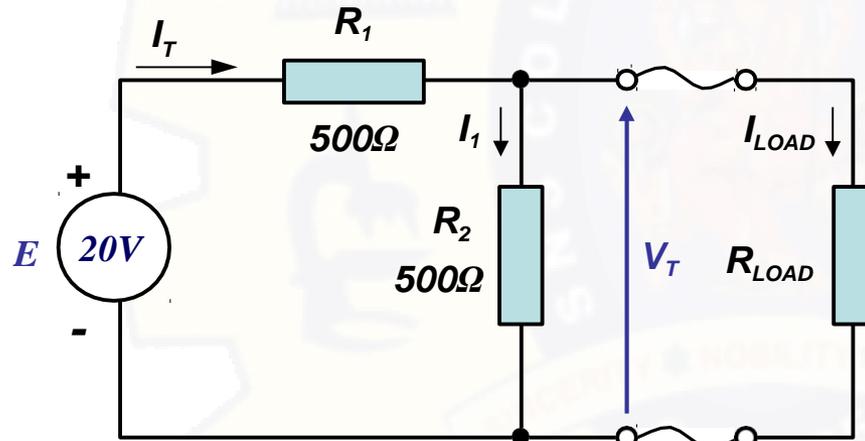
## Activity

*Determine the voltage  $V_T$  under no load conditions and when a resistance of 2000 ohms is connected.*



$V_T$  no load conditions.

$$V_T = E \frac{R_2}{R_1 + R_2}$$

$V_T$  loaded conditions ( $I_{LOAD} \ll I_1$ )

$$V_T \sim E \frac{R_2}{R_1 + R_2}$$


For good stability current  $I_1$  must be at least ten times that flowing in the load.



# Divider Networks

## Activity

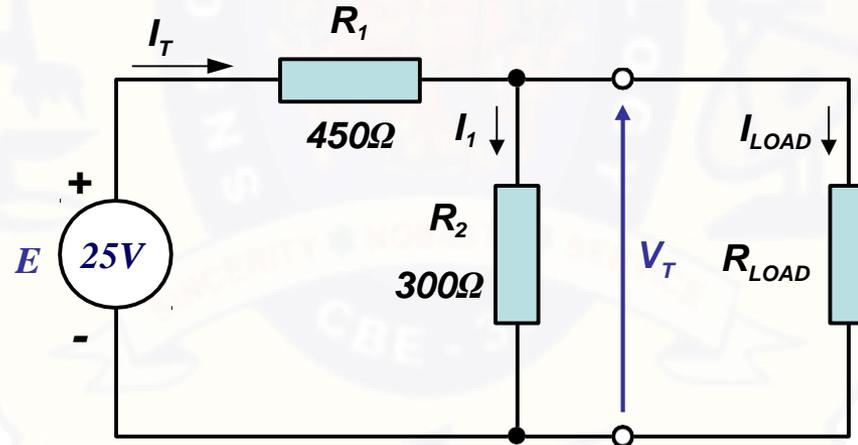1. For the potential divider circuit shown, use the voltage divider principle to evaluate the voltage at  $V_T$  a) when open circuit and b) when a load of  $1000\Omega$  is connected as shown.
2. If the load resistance ( $R_{LOAD}$ ) increased to  $5k\Omega$  what will be the effect on the voltage  $V_T$ .
3. Comment on your results




**What is the effect on the voltage ( $V_T$ ) supplied by the potential divider network as the load ( $R_{LOAD}$ ) varies.**


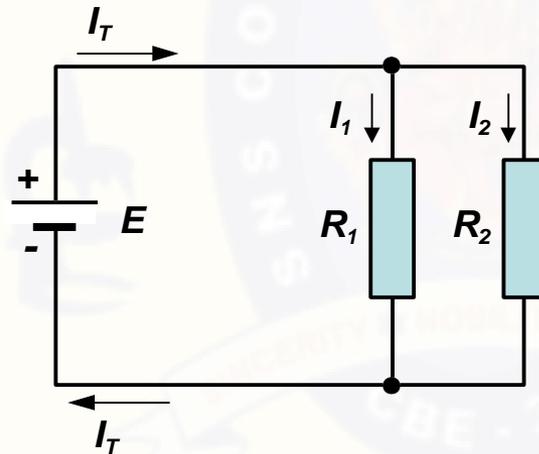
## Current Divider Principle

*In parallel circuits the current  $I_T$  divides up through the various branch networks,  $I_1$ ,  $I_2$ .*

*The ratio between any two branch currents is the inverse ratio of the branch resistances.*



$$I_1 = I_T \frac{R_2}{R_1 + R_2}$$

$$I_2 = I_T \frac{R_1}{R_1 + R_2}$$


*This procedure is only suitable where there are two parallel branches.*


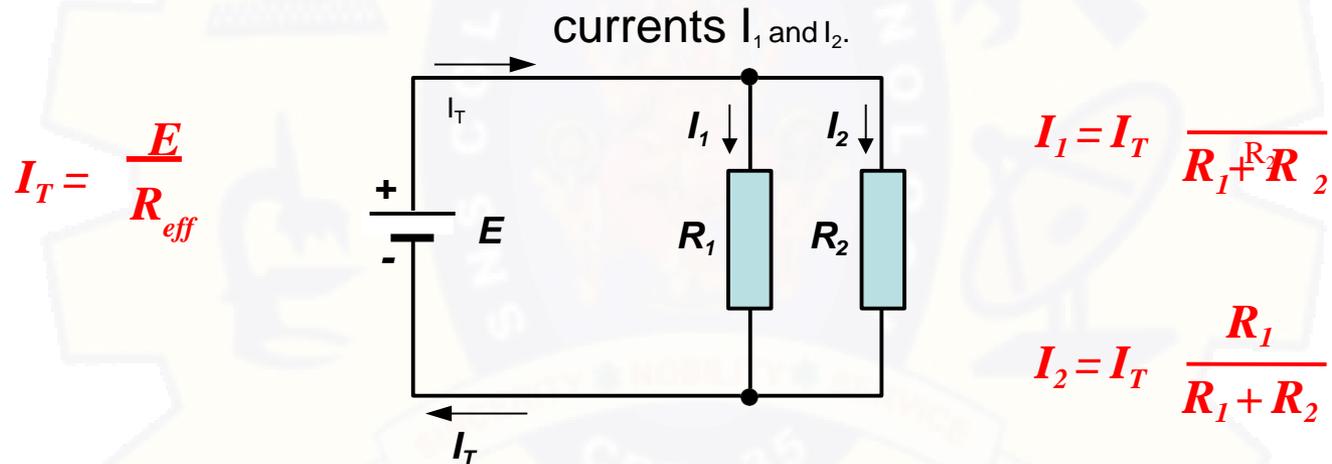
## Current Divider Principle

When there are only two resistances in parallel we can simplify some of the *Ohm's law calculation by use of the current divider principle.*

The current divider uses the principles of Ohm's law to generate the branch




***This procedure is only suitable where there are two parallel branches.***



# Divider Networks

## Activity

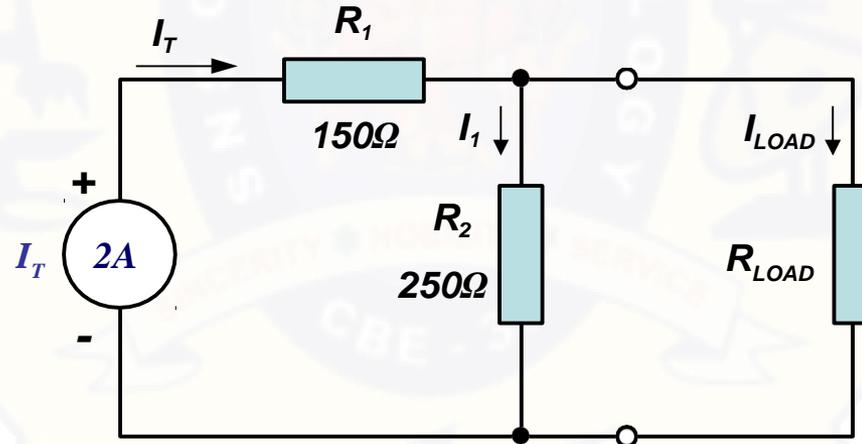1. For the network shown, use the current divider principle to evaluate the branch currents if  $R_{LOAD}$  is  $1000\Omega$ .
2. If the load resistance ( $R_{LOAD}$ ) is reduced to  $500\Omega$  what current will flow in each branch assuming the source current stays the same at  $2A$ .
3. Comment on your results.



**What is the effect on the branch currents supplied by the 2A current source as the load ( $R_{LOAD}$ ) varies.**