



SNS COLLEGE OF TECHNOLOGY

Coimbatore-35
An Autonomous Institution



Accredited by NBA – AICTE and Accredited by NAAC – UGC with 'A++' Grade
Approved by AICTE, New Delhi & Affiliated to Anna University, Chennai

DEPARTMENT OF ELECTRONICS & COMMUNICATION ENGINEERING

23ECB202 – LINEAR INTEGRATED CIRCUITS

II YEAR/ III SEMESTER

UNIT 1 – OP AMP CHARACTERISTICS

TOPIC 1- 8- Slew Rate & Frequency Compensation of Op Amp

2/12/2025




Slew rate



- The slew rate is defined as the maximum rate of change of output voltage caused by a step input voltage.,

Specified in V/ μ s

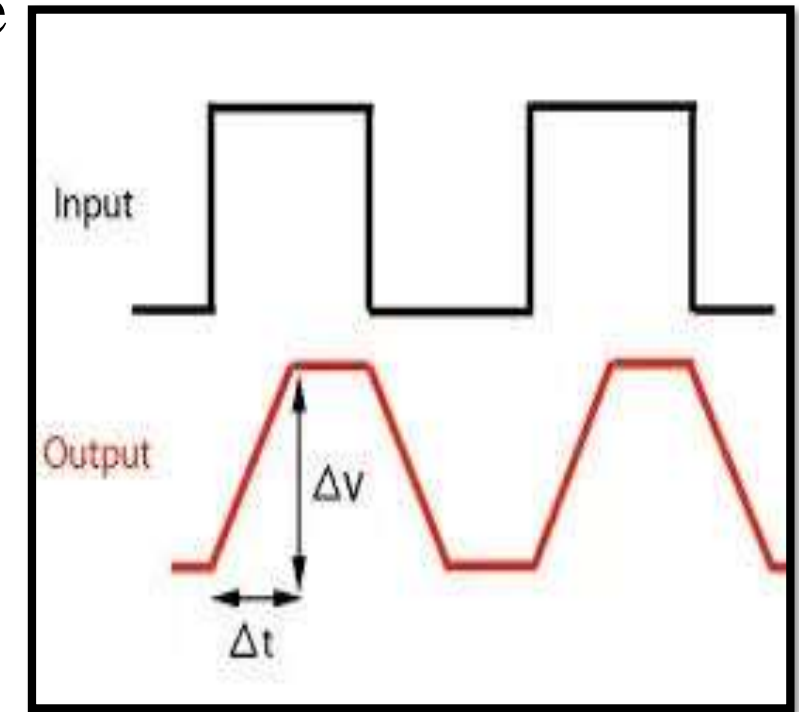eg : 1V/micro sec. slew rate denotes the output rises or falls by 1 volts in 1 micro seconds



- The rate at which the voltage across the capacitor dV_c/dt is given by

$$dV_c/dt = I/C, \text{ Slew rate } SR \ dV_c/dt|_{\max} = I_{\max}/C$$

- For IC741, $I_{\max} = 15$ micro amps, $C = 30$ Pico farad

$$\text{Slew rate} = 0.5V/\text{micro sec}$$



Frequency Compensation of Op Amp



- The major challenge is to improve the stability of an op-amp in a wide bandwidth of applications
- The solution is to compensate the amplifier in terms of frequency response, by using a frequency compensation circuit across the operational amplifier
- The stability of an amplifier is highly dependent on different parameters



Frequency Compensation of Op Amp



Types of Op-Amp Frequency Compensation

- External Frequency Compensation in Op Amp
 1. Dominant pole Compensation
 2. Miller compensation
- Internal Frequency Compensation in Op Amp



External Frequency Compensation in Op Amp



- External compensation techniques vary depending on the application, type of amplifier used and many other things
- The easiest way is to use out-of loop compensation technique or in-loop compensation technique
- Out of the loop compensation technique uses a simple resistor to isolate the capacitive load with the op-amp, lowering the capacitive loading of the op-amp
- The resistor typically varies from 10-50 Ohms but the increase in isolated resistor effects the op-amp bandwidth
- The bandwidth of the op-amp drastically reduced to a very low value. One of the popular ways of out of the loop frequency compensation techniques is to use Dominant pole compensation technique





Dominant pole Compensation

- This technique uses a simple **RC network** connected across the output of the operational amplifier circuit
- This works great to overcome the instability issue
- The RC network creates a pole at unity or 0dB gain that dominates or cancels out other high-frequency poles effect
- The transfer function of the dominant pole configuration

$$A(s) = \frac{A \times \omega_1 \times \omega_2 \times \omega_3}{(s + \omega_1) \times (s + \omega_2) \times (s + \omega_3)}$$

Where,

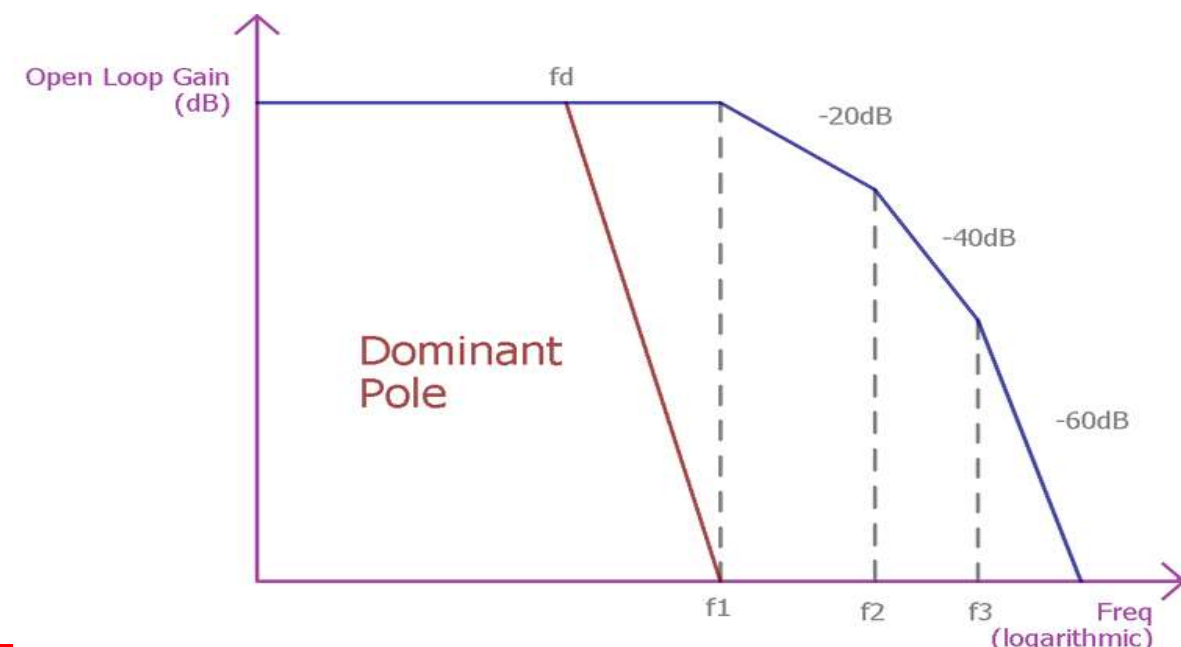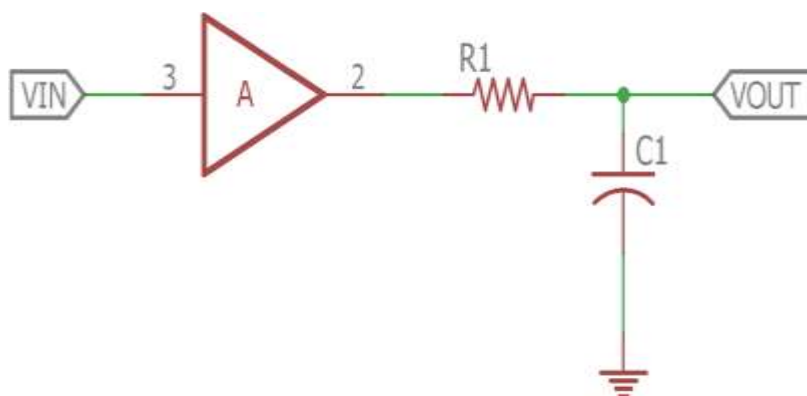
- A(s) is the uncompensated transfer function
- A is the open-loop gain
- ω_1, ω_2 , and ω_3 are the frequencies where the gain roll-off at -20dB, -40dB, -60dB respectively
- The **Bode plot** below shows what happens if the dominant pole compensation technique is added across the op-amp output
- where f_d is the **dominant pole frequency**.





Miller compensation

- Another effective compensation technique is the miller compensation technique and it is an in-loop compensation technique where a simple capacitor is used with or without load isolation resistor (Nulling resistor)
- a capacitor is connected in the feedback loop to compensate the op-amp frequency response
- also , a capacitor is connected to the feedback with a resistor across the output
- The circuit is a simple negative feedback amplifier with inverting gain dependent on R1 and R2
- The R3 is the null resistor and the CL is the capacitive load across the op-amp output
- CF is the feedback capacitor which is used for the compensation purposes
- The Capacitor and the resistor value depend on the type of amplifier stages, pole compensation, and the capacitive load

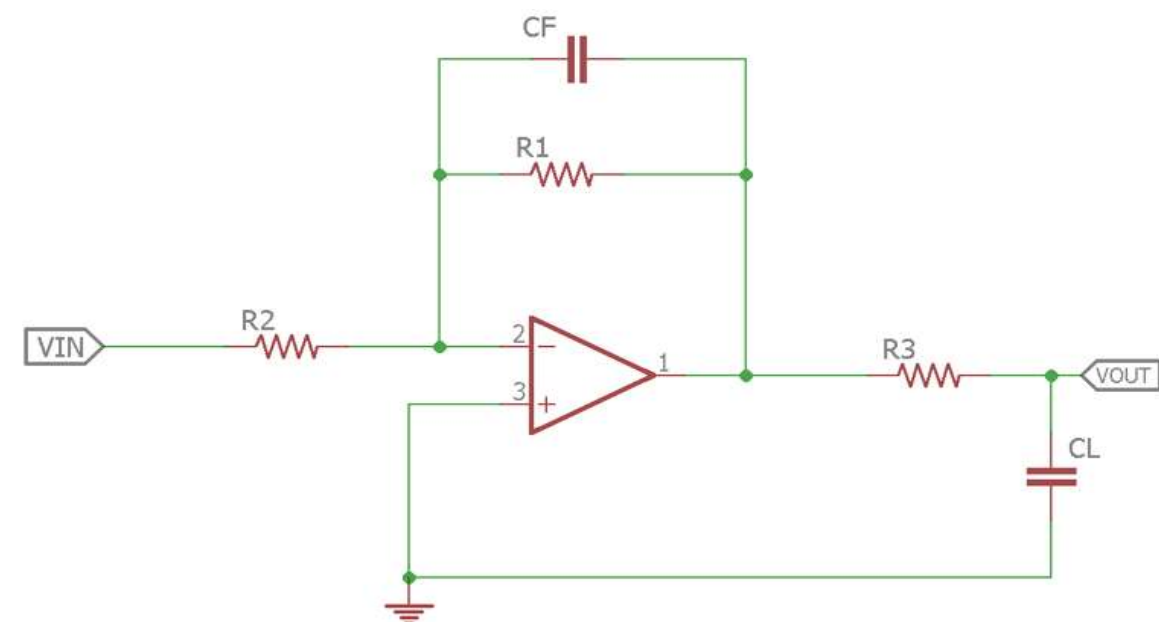




Internal Frequency Compensation Techniques



- Modern operational amplifiers have internal compensation technique
- In the internal compensation technique, a small feedback capacitor is connected inside of the op-amp IC between the second stages Common emitter transistor
- For example, the below image is the internal diagram of popular op-amp LM358
- The C_c capacitor is connected across the Q_5 and Q_{10} . It is the compensation Capacitor (C_c)
- This compensation capacitor improves the stability of the amplifier and as well as prevent the oscillation and ringing effect across the output

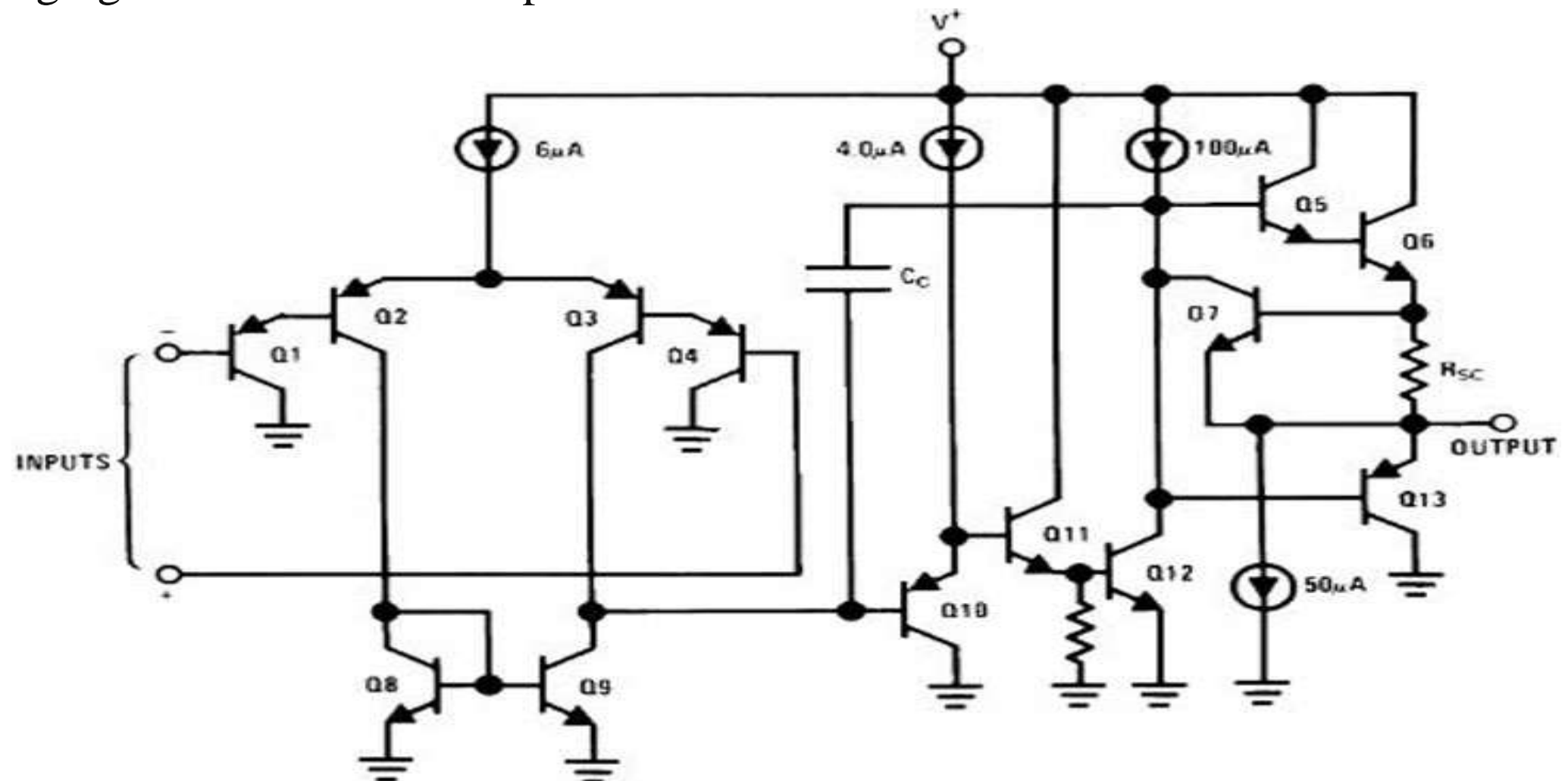



THANK YOU